

# **Alexander-Sadiku**

## **Fundamentals of Electric Circuits**

### **Chapter 1**

### **Basic Concepts**

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



# Basic Concepts - Chapter 1

- 1.1 Systems of Units.
- 1.2 Electric Charge.
- 1.3 Current.
- 1.4 Voltage.
- 1.5 Power and Energy.
- 1.6 Circuit Elements.

## What is an Electric Circuit?

---

- In electrical engineering, we are usually interested in transferring energy or communicating signals from one point to another.


To do this, we often require an interconnection of electrical components.

"An electric circuit is an interconnection of electrical components."


- Typical circuit or electrical components that we will see in this year:  
batteries or voltage sources, current sources, resistors, switches, capacitors, inductors, diodes, transistors, **operational amplifiers**, ...


# A Simple Circuit

---

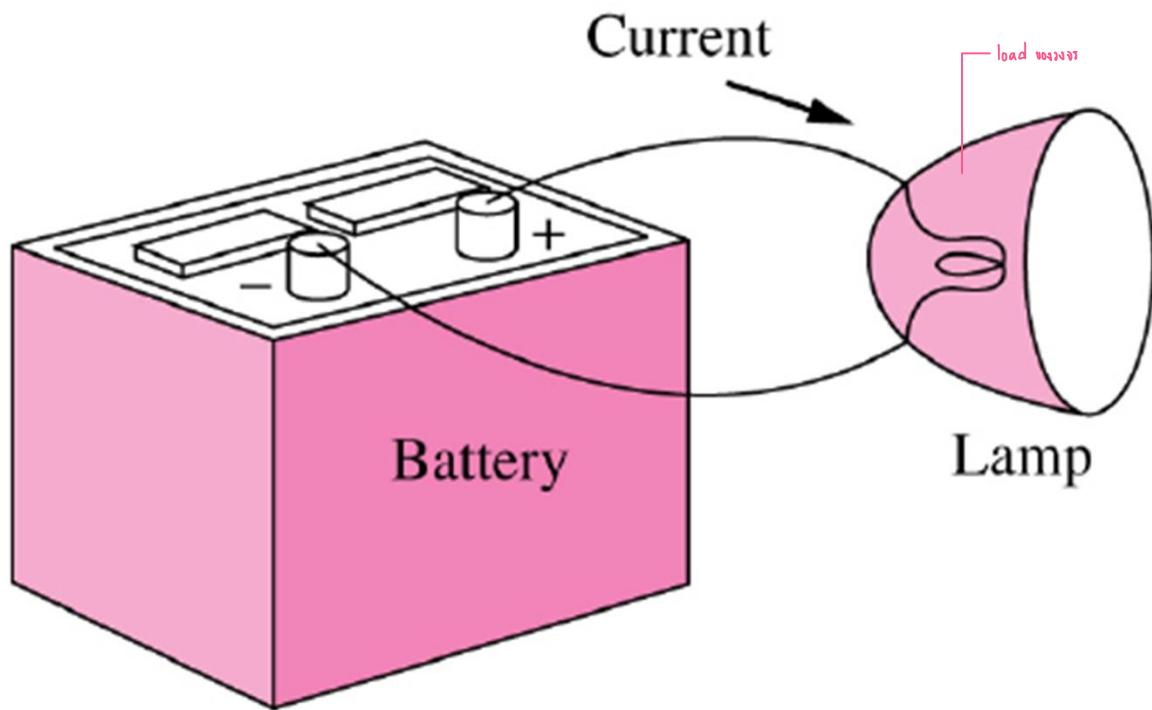

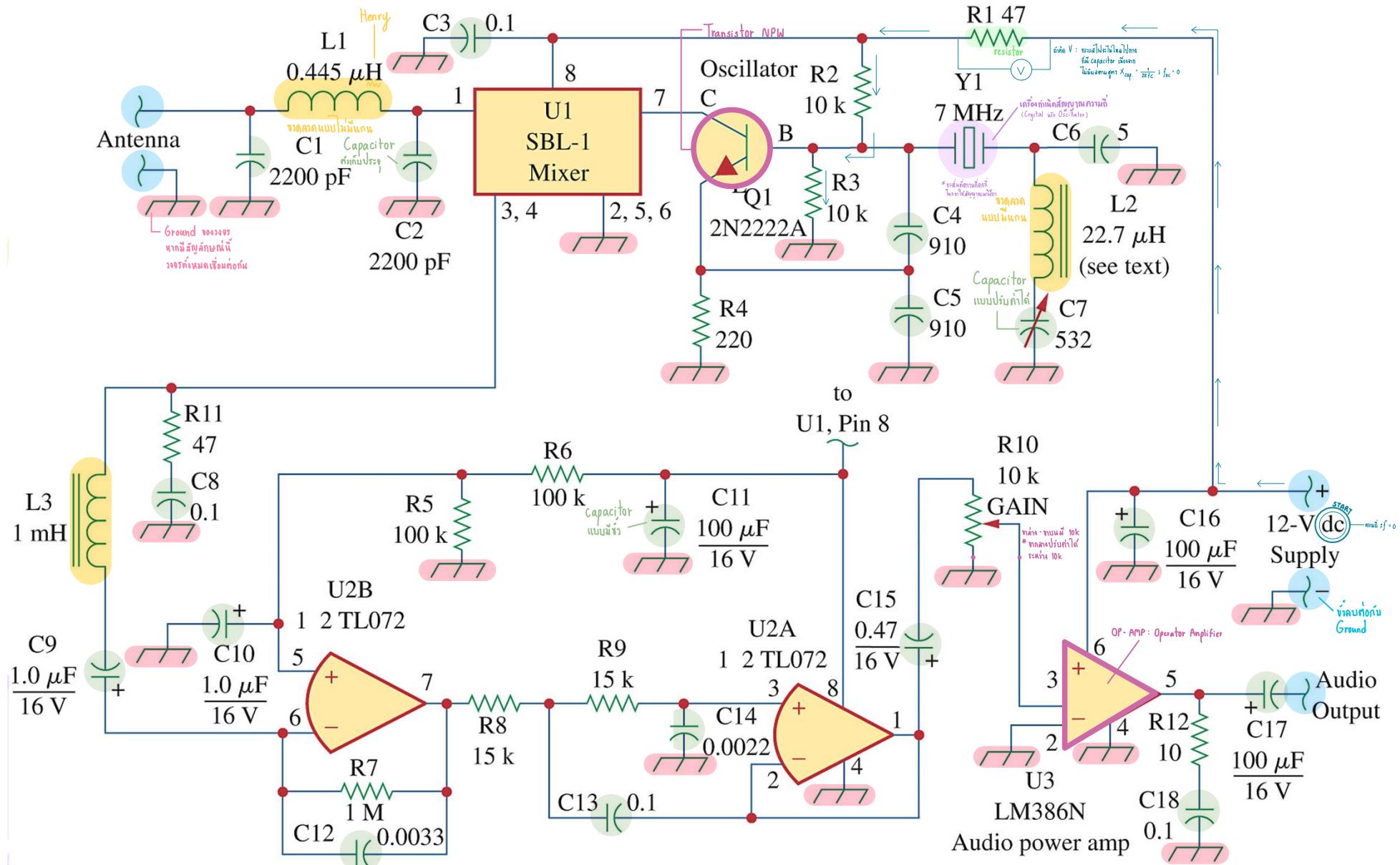Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



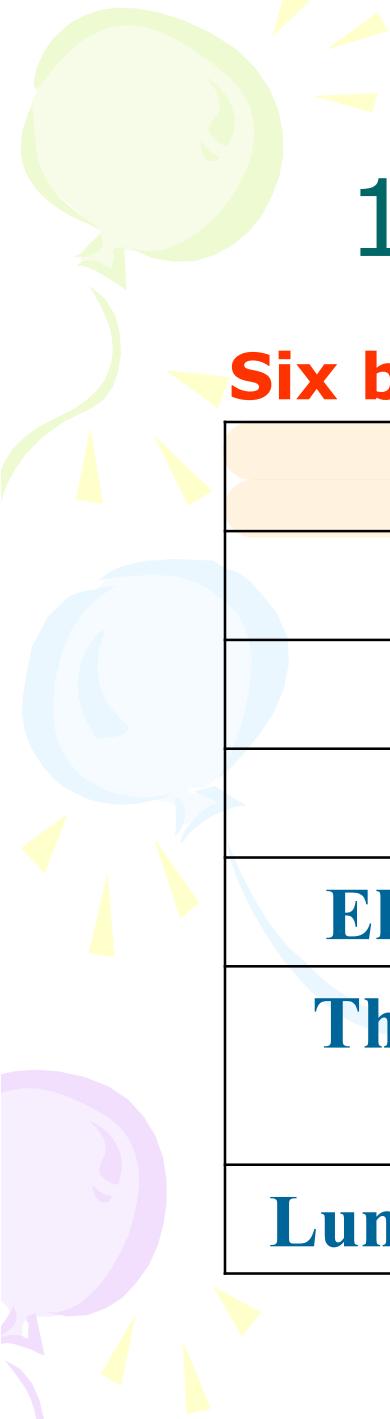

# 1.1 System of Units (1)

## Six basic units

Quantity	Basic unit	Symbol
Length ความยาว	meter	m
Mass น้ำหนัก	kilogram	Kg
Time เวลา	second	s
Electric current กระแสไฟฟ้า	ampere	A
Thermodynamic temperature อุณหภูมิ	K	
Luminous intensity ความเข้มแสง	candela	cd

# 1.1 System of Units (2)

សំណង់របៀបការងារ

**The derived units commonly used in electric circuit theory**

Quantity	Unit	Symbol
electric charge	coulomb	C
electric potential	volt	V
resistance	ohm	$\Omega$
conductance	siemens	S
inductance	henry	H
capacitance	farad	F
frequency	hertz	Hz
force	newton	N
energy, work	joule	J
power	watt	W
magnetic flux	weber	Wb
magnetic flux density	tesla	T

Factor	Prefix	Symbol
$10^9$	giga	G
$10^6$	mega	M
$10^3$	kilo	k
$10^{-2}$	centi	c
$10^{-3}$	milli	m
$10^{-6}$	micro	$\mu$
$10^{-9}$	nano	n
$10^{-12}$	pico	p


**Decimal multiples and  
submultiples of SI units**



## 1.2 Electric Charges


- Charge is an electrical property of the atomic particles of which matter consists, measured in coulombs (C).
- The charge  $e$  on one electron is negative and equal in magnitude to  $1.602 \times 10^{-19}$  C which is called as electronic charge. The charges that occur in nature are integral multiples of the electronic charge.

## 1.3 Current

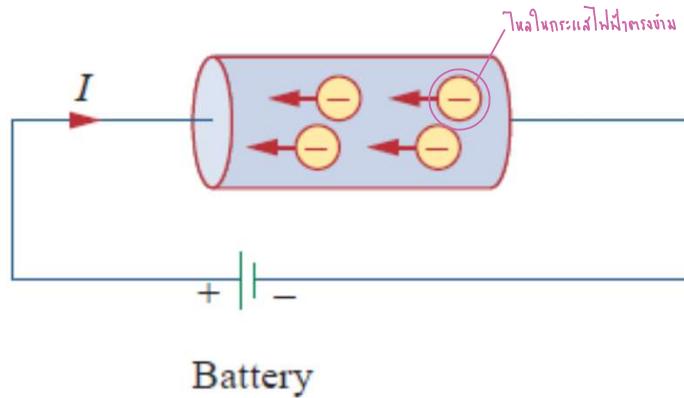


- Electric current  $i = dq/dt$ .
- The unit of ampere can be derived as  
1 Ampere = 1 Coulomb/second.

# 1.3 Direct Current

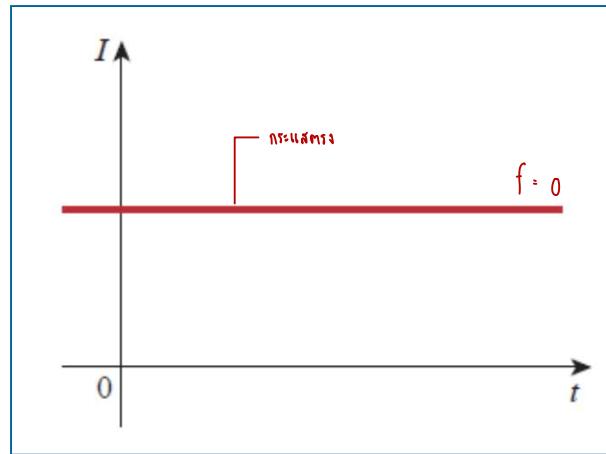


- A **direct current (dc)** is a current that remains constant with time.

# 1.3 Alternating Current

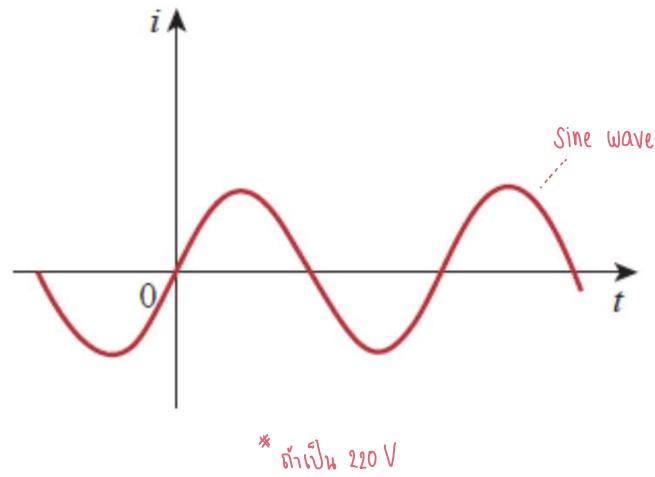


- An alternating current (ac) is a current that varies sinusoidally with time. (reverse direction)

# 1.3 Current Flow

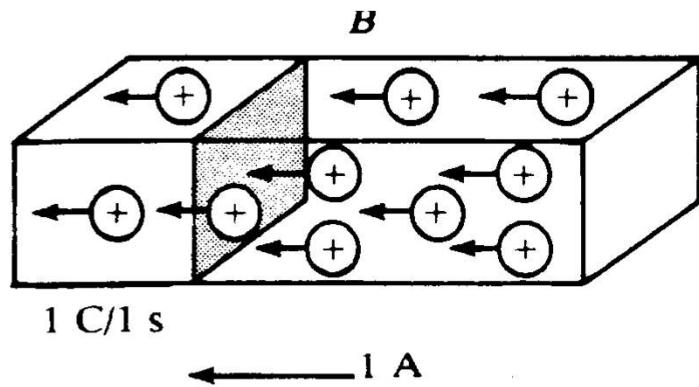

(a)

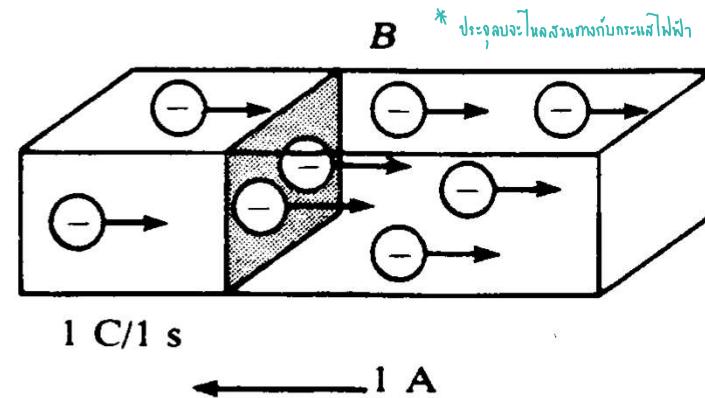


(b)

Positive ions

Negative ions

# 1.3 Current Flow

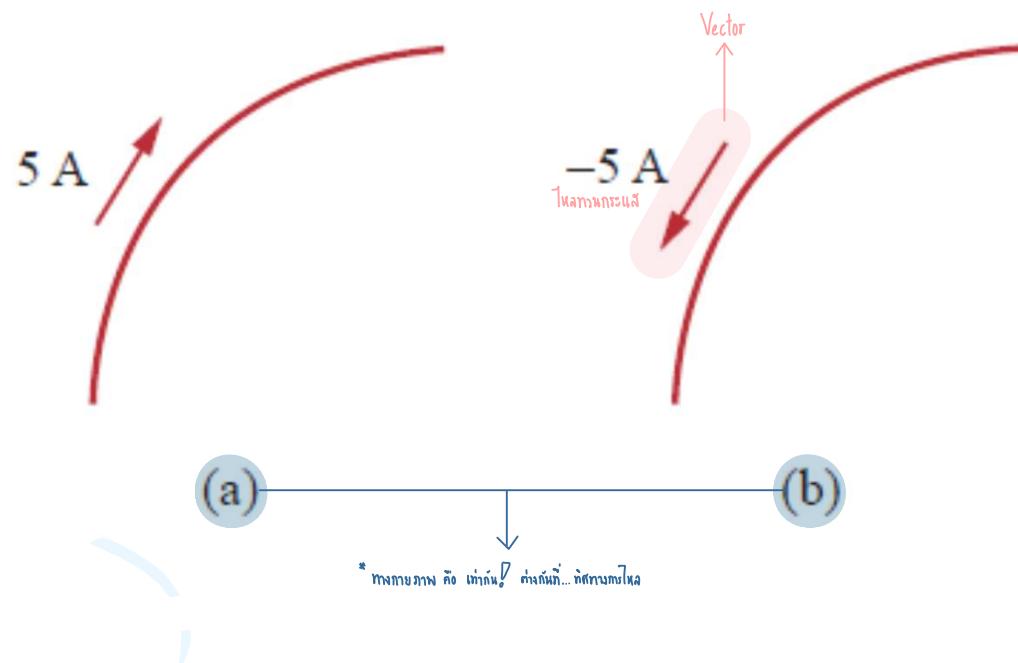

# 1.3 Current


## Example 1

How much charge represented by 4,600 electrons? ;  $e^- = 1.602 \times 10^{-19}$

ກະລຸ

$$4600 \text{ electrons} \times 1.602 \times 10^{-19} \text{ C/electrons}$$

$$= 7.369 \times 10^{-16}$$

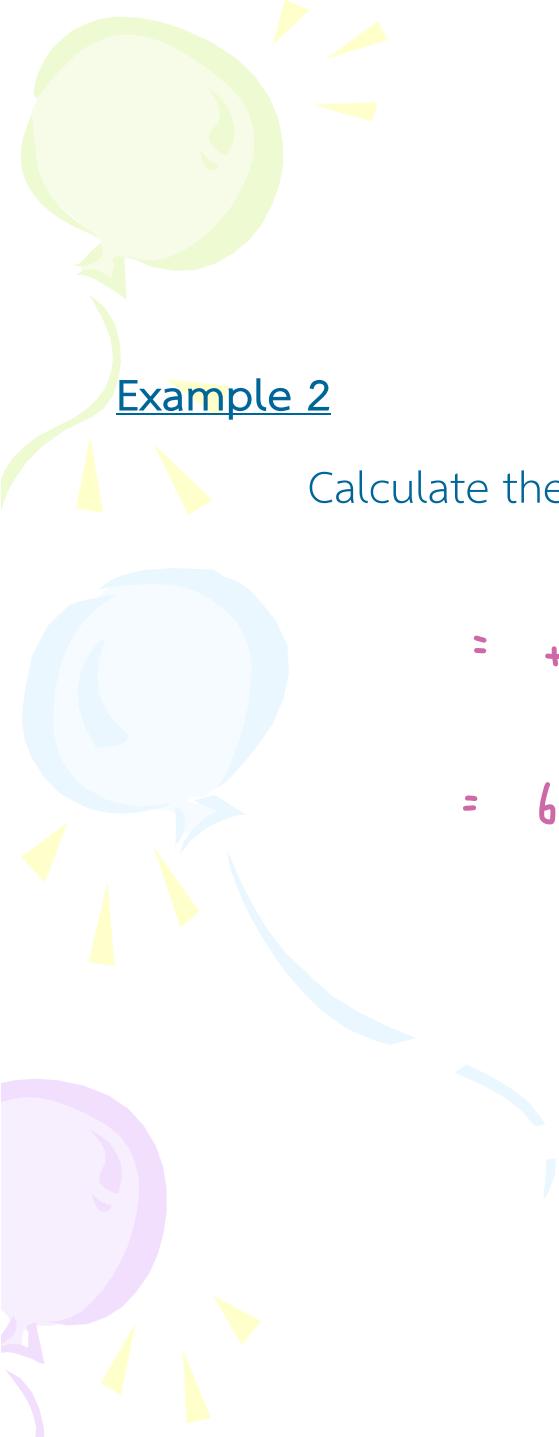

## 1.3 Current

### Example 2

Calculate the amount of charge represented by  $4 \times 10^6$  four million protons.

$$\begin{aligned} &= +1.602 \times 10^{-19} \times 4 \times 10^6 \\ &= 6.408 \times 10^{-33} \end{aligned}$$

# 1.3 Current

## Example 3

The total charge entering a terminal is given by  $q = 5t \sin 4\pi t$  mC.

Calculate the current at  $t=0.5$  s.

$$i = \frac{dq}{dt} = \frac{d}{dt}(5t \sin 4\pi t) \text{ mC/s} = (5 \sin 4\pi t + 20\pi t \cos 4\pi t) \text{ mA}$$

At  $t = 0.5$ ,

$$i = 5 \sin 2\pi + 10\pi \cos 2\pi = 0 + 10\pi = 31.42 \text{ mA}$$


## C.4

## Derivatives

If  $U = U(x)$ ,  $V = V(x)$ , and  $a = \text{constant}$ ,

$$\frac{d}{dx}(aU) = a \frac{dU}{dx}$$
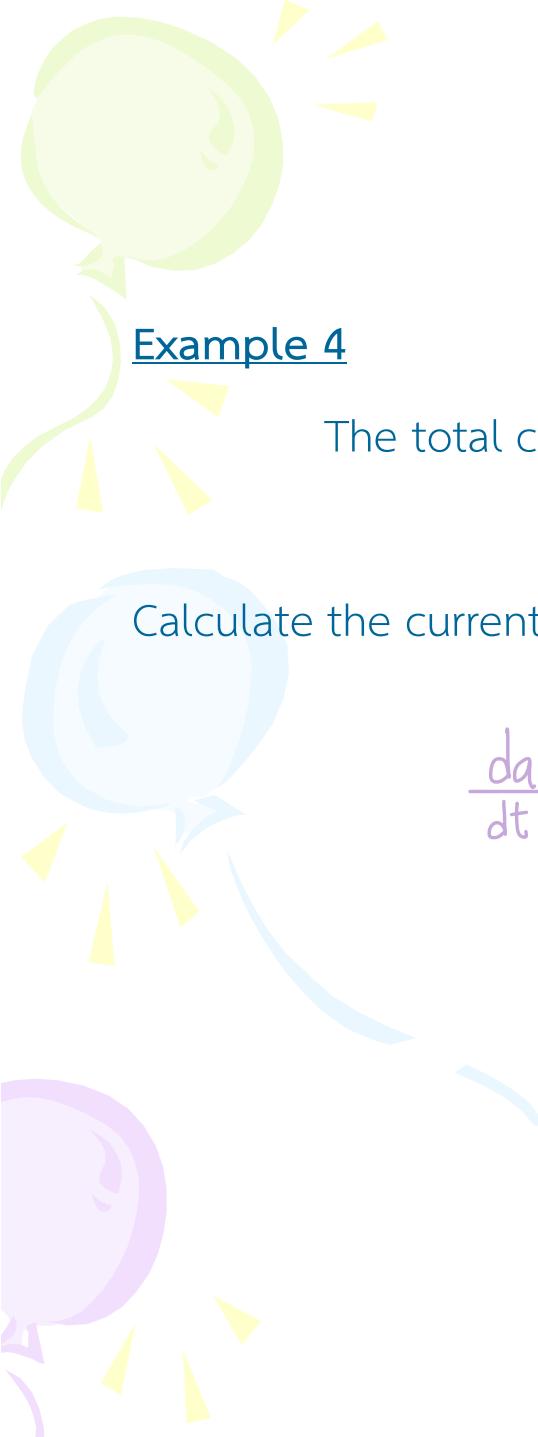
$$\frac{d}{dx}(UV) = U \frac{dV}{dx} + V \frac{dU}{dx}$$



# 1.3 Current

## Example 4

The total charge entering a terminal is given by

$$q = (10 - 10e^{-2t}) \text{ mC}$$

Calculate the current at t=0.5 s.

$$\begin{aligned}\frac{da}{dt} &= (10 - 10e^{-2t}) \\&= 20e^{-2t} \\&= 20e^{-2(0.5)} \\&\quad \boxed{1.602 \times 10^{-16}} \\&= \frac{20}{2.7} \\&= 7.36 \text{ mA}\end{aligned}$$

$$\frac{d}{dx}\left(\frac{U}{V}\right) = \frac{V\frac{dU}{dx} - U\frac{dV}{dx}}{V^2}$$

$$\frac{d}{dx}(aU^n) = naU^{n-1}$$

$$\frac{d}{dx}(a^U) = a^U \ln a \frac{dU}{dx}$$

$$\frac{d}{dx}(e^U) = e^U \frac{dU}{dx}$$

$$\frac{d}{dx}(\sin U) = \cos U \frac{dU}{dx}$$

$$\frac{d}{dx}(\cos U) = -\sin U \frac{dU}{dx}$$

# 1.3 Current

## Example 5

Determine the total charge entering a terminal between  $t=1$  s and  $t=2$  s if the current passing the terminal is  $i = (3t^2 - t)$  A.

$$\begin{aligned} i &= \frac{dQ}{dt} \\ Q &= \int i dt \\ &= \int_1^2 (3t^2 - t) dt \\ &= \left( t^3 - \frac{t^2}{2} \right) \Big|_1^2 \\ &= \left[ (2)^3 - \frac{2^2}{2} \right] - \left[ (1)^3 - \frac{1^2}{2} \right] \\ &= 6 - \frac{1}{2} \\ &= 5.5 C \end{aligned}$$

# 1.3 Current

## Example 6

$$\begin{aligned} * 1 \text{ A} &= 1 \text{ C/sec} \\ &= 60 \text{ C/min} \end{aligned}$$

A conductor has a constant current of 5 A. How many electrons pass a fixed point on the conductor in one minute?

$$\frac{300 \text{ C/min}}{1.602 \times 10^{-19} \text{ C/electronic}} = 1.87 \times 10^{21} \frac{\text{electronic}}{\text{min}}$$

# 1.3 Current

## Example 6

A conductor has a constant current of 5 A. How many electrons pass a fixed point on the conductor in one minute?

$$\frac{300 \text{ C/min}}{1.602 \times 10^{-19} \text{ C/electron}} = 1.87 \times 10^{21} \text{ electrons/min}$$

## 1.3 Current

### Example 7

ถ้าประจุไฟฟ้าเคลื่อนที่ผ่านตัวนำ 900 Coulombs ในเวลา 1.5 นาที จะมีกระแสไฟฟ้าไหลผ่าน กี่แอมเปอร์

$$\frac{1}{90 \text{ Sec}}$$

10 A

# 1.3 Current

## Example 8

อิเล็กตรอนอิสระเคลื่อนที่ในโลหะตัวนำ โดยใน 2 วินาทีจะเคลื่อนผ่านพื้นที่หน้าตัดแห่งหนึ่ง  $4 \times 10^{10}$  ตัว จงหากระแสไฟฟ้าที่ผ่านตัวนำนี้


$$4 \times 10^{10} \times (1.602 \times 10^{-19})$$

$$= 3.204 \times 10^{-9} \text{ A}$$

## 1.3 Current

Example 9

จงเขียนกราฟ ของกระแสและเวลา

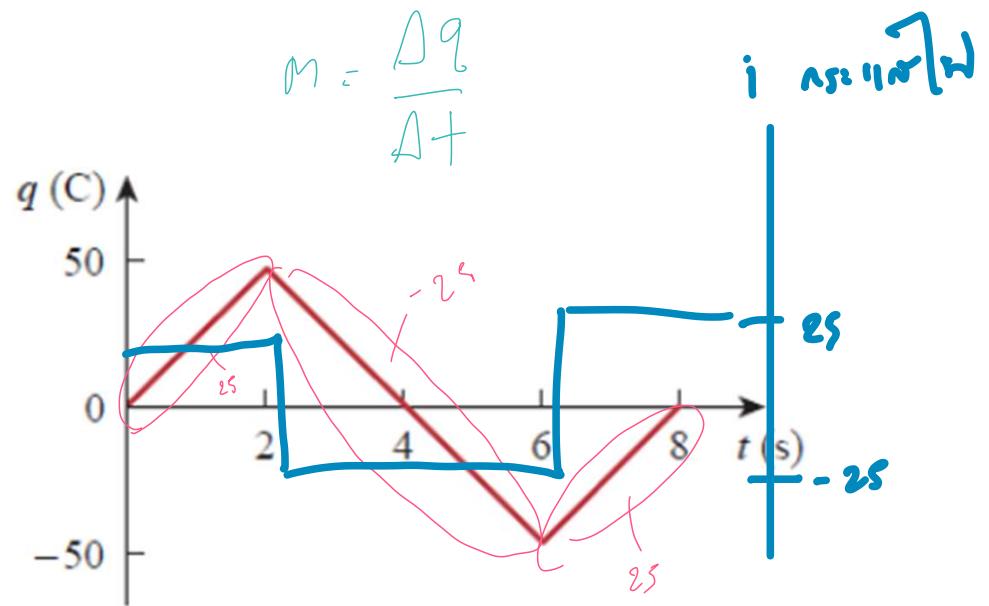



มีความต่างศักย์แรงงานเท่าๆ กัน 2 จุด

## 1.4 Voltage

\* 1 โคลอมบ์

- Voltage (or potential difference) is the **energy** required to move **a unit charge** through an element, measured in volts (V).


$$v_{ab} \triangleq \frac{dw}{dq}$$

- $w$  is energy in joules (J) and  $q$  is charge in coulomb (C).

$$1 \text{ volt} = 1 \text{ joule/coulomb} = 1 \text{ newton-meter/coulomb}$$
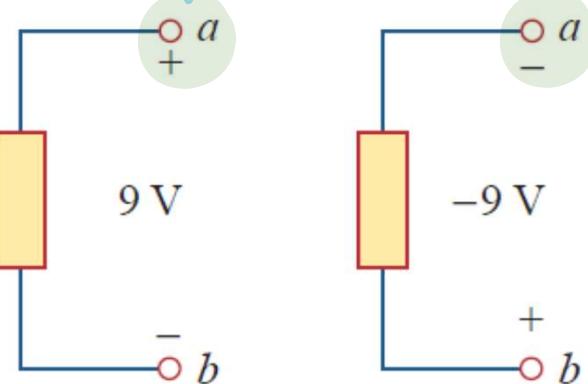
# 1.4 Voltage

- Electric voltage,  $v_{ab}$ , is always across the circuit element or between two points in a circuit.
  - $v_{ab} > 0$  means the potential of **a** is higher than potential of **b**.
  - $v_{ab} < 0$  means the potential of **a** is lower than potential of **b**.



$$v_{ab} = -v_{ba}$$

## 1.4 Voltage

### Example 1

ถ้าความต่างศักย์ระหว่าง 2 จุดมีค่าเท่ากับ 42 V จงหาค่าของงานที่ต้องการในการนำประจุขนาด 6 C จากจุดหนึ่งไปยังอีกจุดหนึ่ง

$$V_{ab} = \frac{\Delta W}{\Delta C}$$

$$42 \text{ V} = \frac{W}{6 \text{ C.}}$$
$$= 252 \text{ J.}$$


## 1.4 Voltage

### Example 2

แรงดันของแบตเตอรี่ควรจะมีค่าเท่าใดโดยที่แบตเตอรี่ซึ่งใช้พลังงาน 800 J ใน การเคลื่อนย้ายประจุจำนวน 40 C ผ่านความต้านทาน

$$V = \frac{\Delta W}{\Delta Q}$$
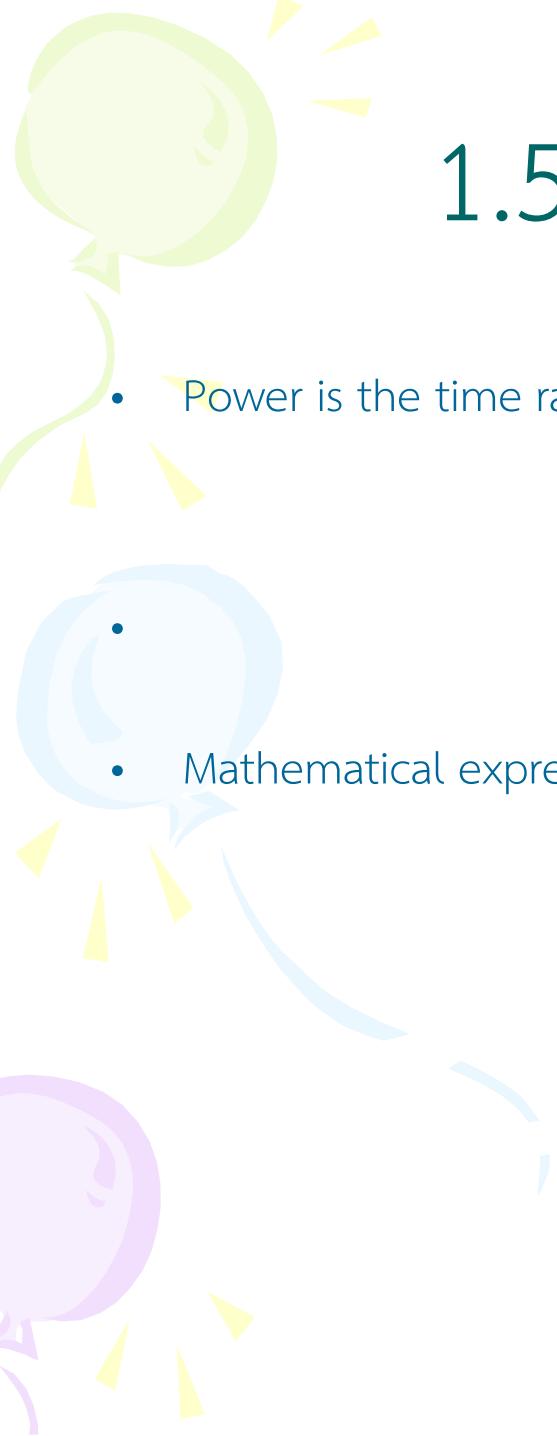
$$= \frac{800 \text{ J}}{40 \text{ C}}$$
$$= 20 \text{ V}$$



## 1.5 Power and Energy


- Power is the time rate of expending or absorbing energy, measured in watts (W).
- Mathematical expression:

$$p \triangleq \frac{dw}{dt}$$

$$p = \frac{dw}{dt} = \frac{dw}{dq} \cdot \frac{dq}{dt} = vi$$

$$p = vi$$


# 1.5 Power and Energy

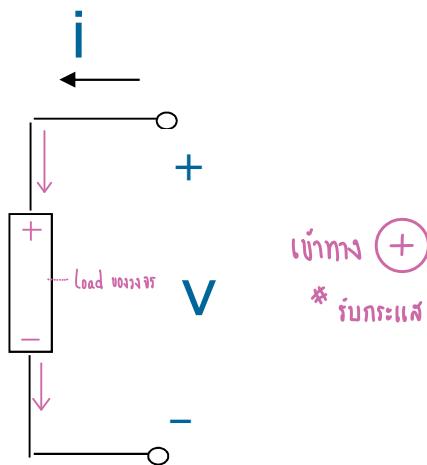

$$P = +vi$$

absorbing power

\* รับพลังงาน

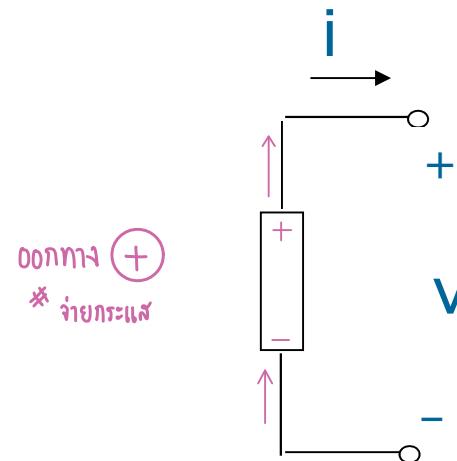


$$P = -vi$$

supplying power


\* ให้พลังงาน

# 1.5 Power and Energy


$$P = VI$$

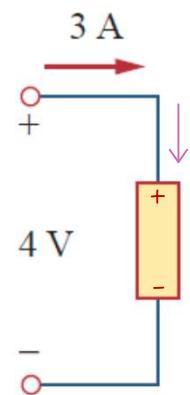


A = +12 A

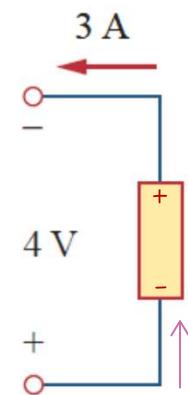

B = +12 A

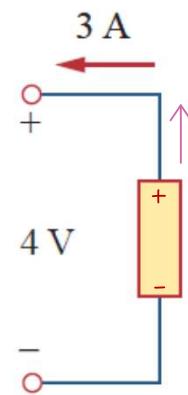

C = -12 A

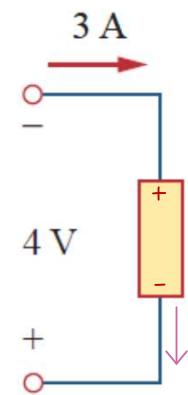

D = -12 A



## 1.5 Power and Energy (2)

กฎอนุรักษ์พลังงาน

- The law of conservation of energy

$$\sum p = 0 \quad * \text{ไม่สูญเสียแต่เปลี่ยนรูป}$$

- Energy is the capacity to do work, measured in joules (J).

- Mathematical expression  $w = \int_{t_0}^t pdt = \int_{t_0}^t vidt$

# 1.5 Power and Energy

## Example 1

$$i = 2 \text{ A}, t = 10 \text{ sec}, W = 2.3 \text{ kJ}, V = 2V$$

An energy source forces a constant current of 2 A for 10 s to flow through a lightbulb. If 2.3 kJ is given off in the form of light and heat energy, calculate the voltage drop across the bulb.

$$W = \int Vi dt$$

$$V = \frac{1}{i} \cdot \frac{dW}{dt} = \frac{1}{2 \text{ A}} \cdot \frac{2.3 \times 10^3 \text{ J}}{10 \text{ sec}}$$

$$= 115 \text{ V}$$

# 1.5 Power and Energy

## Example 2

W អត់ងារ

To move charge  $q$  from point  $a$  to point  $b$  requires  $\text{---}30 \text{ J}$ . Find the voltage drop  $v_{ab}$  if: (a)  $q = 2 \text{ C}$ , (b)  $q = -6 \text{ C}$ .

$$\Delta V_{ab} = \frac{\Delta W}{\Delta C}$$

(a) ;  $\frac{-30 \text{ J}}{2 \text{ C}} = -15 \text{ V}$ .

(b) ;  $\frac{-30 \text{ J}}{-6 \text{ C}} = +5 \text{ V}$ .

## 1.5 Power and Energy


### Example 3

Find the power delivered to an element at  $t = 3$  ms if the current entering its positive terminal is

$$i = 5 \cos 60\pi t \text{ A}$$

and the voltage is: (a)  $v = 3i$ , (b)  $v = 3 di/dt$ .

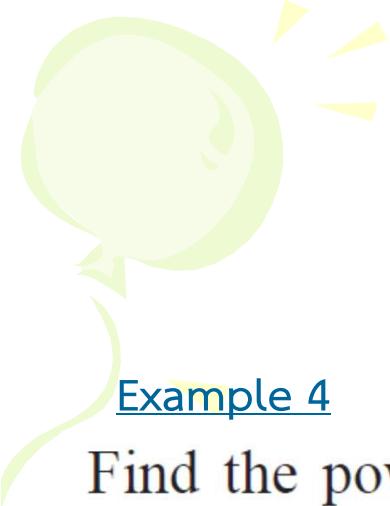
$$\begin{aligned} & 3 \left( \frac{di}{dt} \right) \cos 60\pi (3) \\ &= 3 \left( \frac{15\pi}{2} \right)^3 \end{aligned}$$



## 1.5 Power and Energy
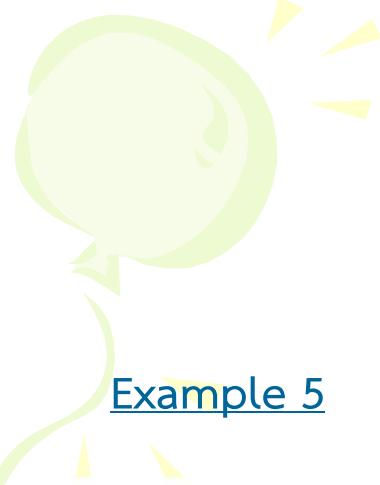
### Example 4

Find the power delivered to the element in Example 3 at  $t = 5$  ms if the current remains the same but the voltage is: (a)  $v = 2i$  V,



## 1.5 Power and Energy


### Example 5

$$2 \times 10^6$$

How much energy does a 100-W electric bulb consume in two hours?


$$P = 50$$



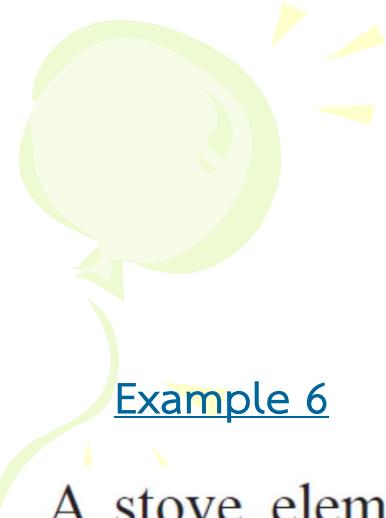

### Example 6

A stove element draws 15 A when connected to a 240-V line. How long does it take to consume 60 kJ?



$$P = \frac{W}{t} = V I$$
$$= I^2 R = \frac{V^2}{R}$$

$$V I = 3600$$

$$I = 15A$$

$$V = 240V$$

$$\text{want } W = 60 \text{ kJ}$$

$$t = \frac{Q}{I}$$

$$= \frac{W}{P}$$

$$\frac{W}{t} = V I$$

$$\frac{60 \times 10^3}{E} = 3600$$

$$t = \frac{600 \times 10^3}{3600}$$
$$= 6$$






## 1.5 Power and Energy
 
### Example 7

จงหาพลังงานที่ใช้ เมื่อหลอดไฟ 60 W ใช้ไปในเวลา 2 ชั่วโมง



30 W

## 1.5 Power and Energy


### Example 8

จงหาจำนวนของอิเล็กตรอนต่อวินาทีที่ไหลผ่านหลอดไฟเมื่อหลอดไฟนั้นต่ออยู่กับแหล่งจ่ายแรงดันขนาด 120 V โดยที่หลอดไฟดังกล่าวมีขนาด 75 W

# 1.5 Power and Energy
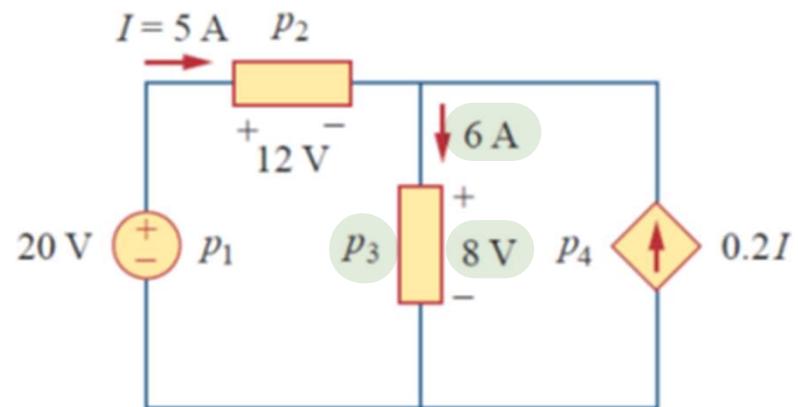
## Example 9

กำลังงานดูดกลืน (absorbed power) ที่ต้องการโดย อุปกรณ์ P3 คือเท่าใด





$$\begin{aligned}P_3 &= VI \\&= 8 \text{ V} \times 6 \text{ A} \\&= 48 \text{ V}\end{aligned}$$

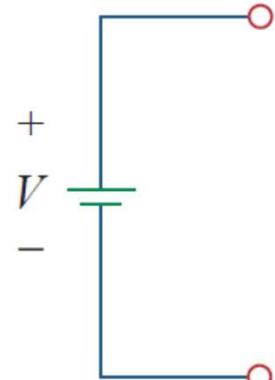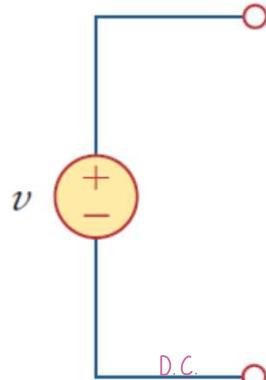
# 1.6 Circuit Elements

ແລ້ວກໍເນັດວ່າສະໝັກນັດໄວ

An **ideal independent source** is an active element that provides a specified voltage or current that is completely independent of other circuit elements.



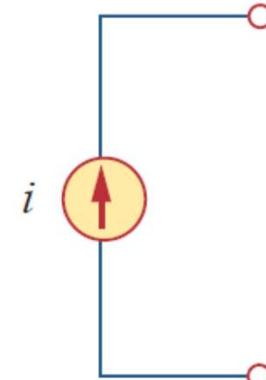voltage source  
ແລ້ວກໍເນັດ; ແລ້ວຈ່າຍພລົງຈານ




current source
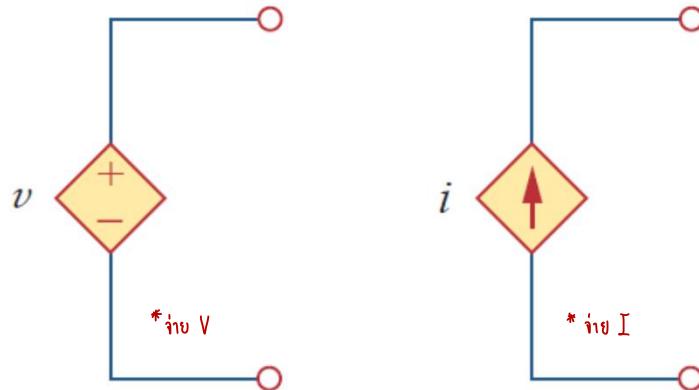
# 1.6 Circuit Elements

ແລ້ວກຳນົດຮູ່ເພັນກັບຕົ້ນ

An **ideal dependent** (or **controlled**) source is an active element in which the source quantity is controlled by another voltage or current.




- V ກຳນົດ  
I ກຳນົດ
- 1. A voltage-controlled voltage source (VCVS).  
2. A current-controlled voltage source (CCVS).  
3. A voltage-controlled current source (VCCS).  
4. A current-controlled current source (CCCS).
- I : ກະລຸສິໄສ




# 1.6 Circuit Elements

ຈ່າຍພລ່ງງານ


## Active Elements

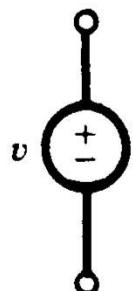

(a)

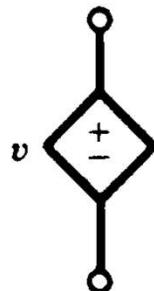

(b)

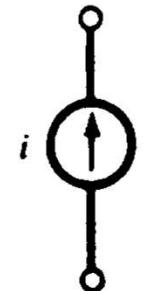

(c)



(d)

ຮັບພລ່ງງານ


## Passive Elements



(e)



(f)

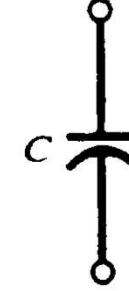

(g)


Independent sources      Dependant sources

- A dependent source is an active element in which the source quantity is controlled by another voltage or current.
- They have four different types: VCVS, CCVS, VCCS, CCCS. Keep in minds the signs of dependent sources.

# 1.6 Circuit Elements

## Example 1

จากรูป V มีค่าเท่าใด

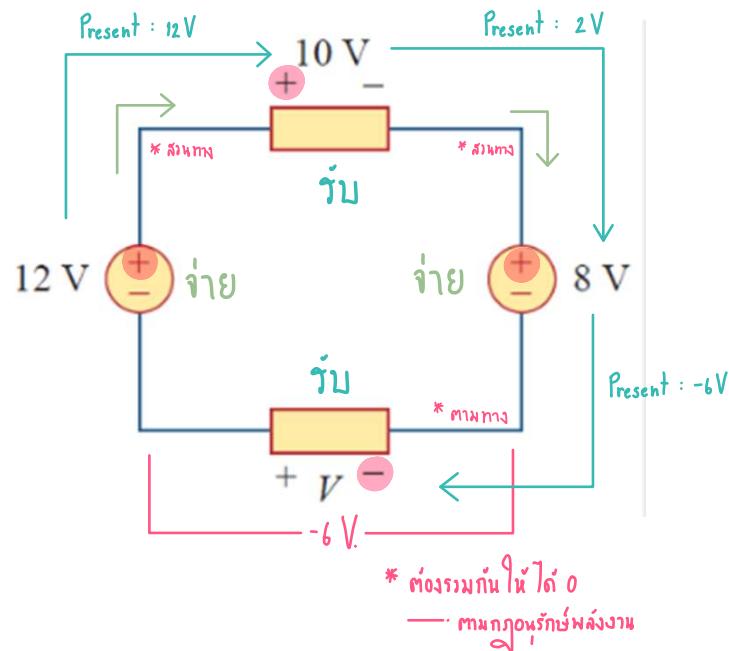


## 1.6 Circuit Elements
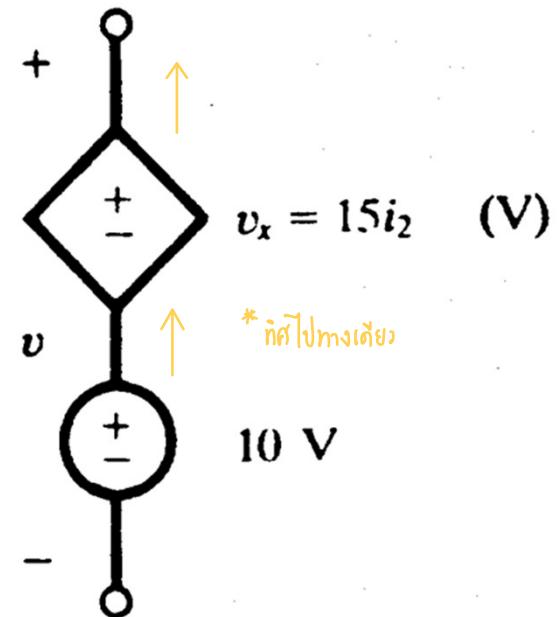
### Example 2

$$i_2 = 1A$$


V มีค่าเท่าใด  
└─ งาน  $V_{AII}$  ได้ 25 V.



$$P = VI$$

## 1.6 Circuit Elements

Example 3

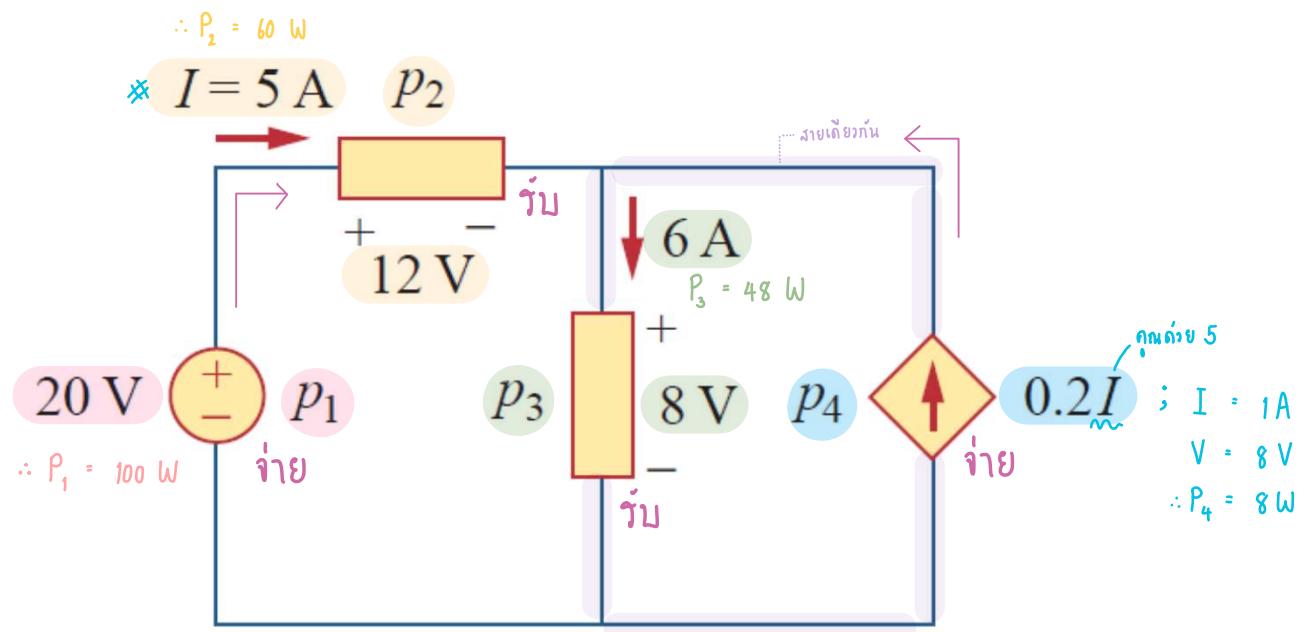


Calculate the power supplied or absorbed by each element

## 1.6 Circuit Elements
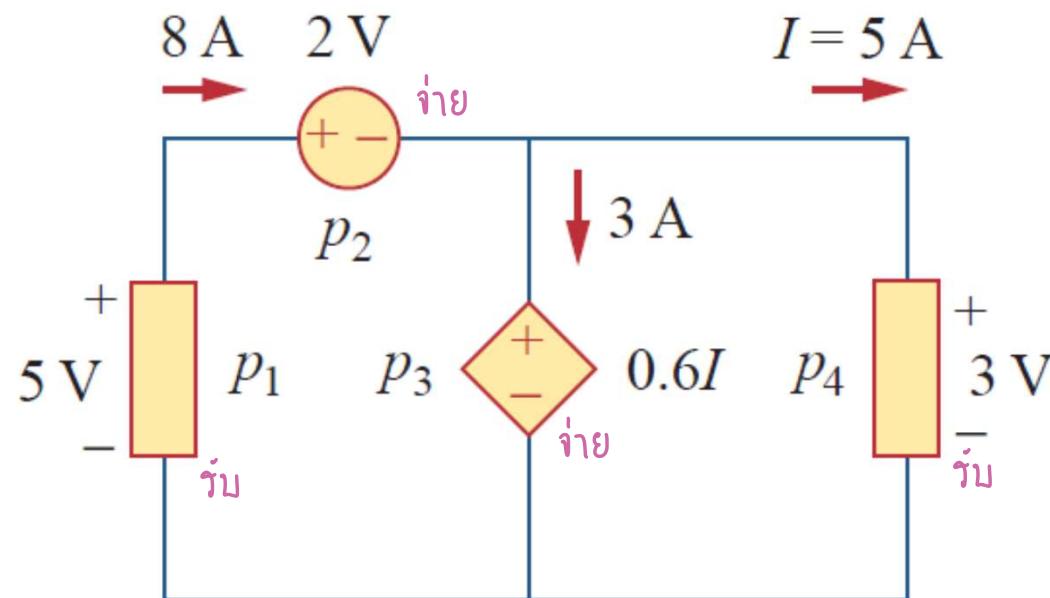
### Example 4

\*  : อยู่ทิ้งหอก เป็น "รบ"  
อยู่ทิ้งใน เป็น "รบ"



Compute the power absorbed or supplied by each component