

The background features several large, overlapping, curved shapes in light green, light blue, and light purple. Scattered throughout are numerous small, yellow, triangular shapes, some pointing towards the center and others away from it, creating a dynamic, starburst-like effect.

# **Alexander-Sadiku**

## **Fundamentals of Electric Circuits**

### **Chapter 6**

### **Capacitors and Inductors**

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



# Capacitors and Inductors

## Chapter 6

6.1 Capacitors



6.2 Series and Parallel Capacitors

6.3 Inductors

6.4 Series and Parallel Inductors
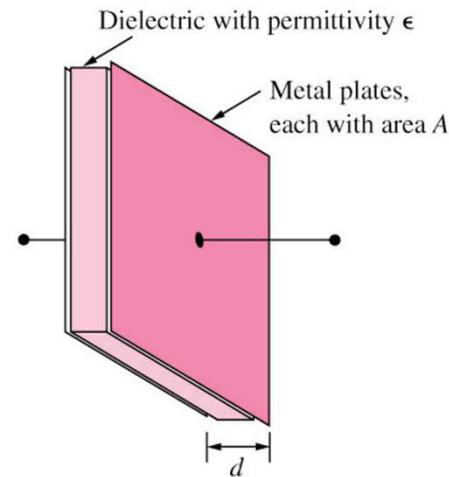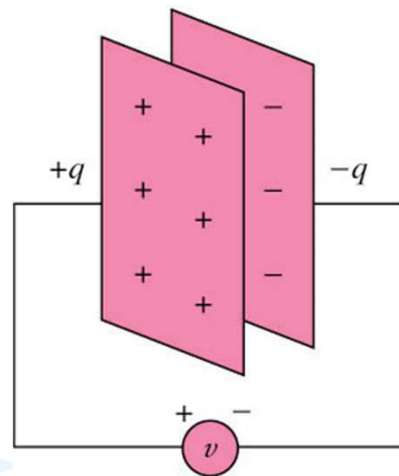
## 6.1 Capacitors (1)


- A capacitor is a passive element designed to **store energy** in its **electric field**.



- A **capacitor** consists of two conducting plates separated by an insulator (or dielectric).
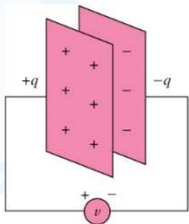
## 6.1 Capacitors (2)

- **Capacitance**  $C$  is the ratio of the charge  $q$  on one plate of a capacitor to the voltage difference  $v$  between the two plates, measured in farads (F).



$$q = C v$$

and

$$C = \frac{\epsilon A}{d}$$


- Where  $\epsilon$  is the permittivity of the dielectric material between the plates,  $A$  is the surface area of each plate,  $d$  is the distance between the plates.
- Unit: F, pF ( $10^{-12}$ ), nF ( $10^{-9}$ ), and  $\mu\text{F}$  ( $10^{-6}$ )

## 6.1 Capacitors (3)

- If  $i$  is flowing into the +ve terminal of C

การทำงานของ Capacitor มี 2 อย่าง

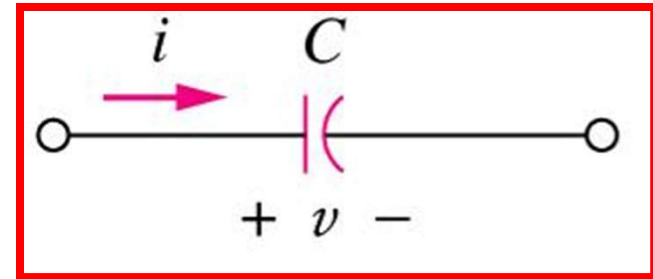- - Charging  $\Rightarrow i$  is +ve
- - Discharging  $\Rightarrow i$  is -ve



- The current-voltage relationship of capacitor according to above convention is

$$i = C \frac{d v}{d t}$$

อัตราการเปลี่ยนแปลงความต่างศักย์เทียบกับเวลา

and


$$v = \frac{1}{C} \int_{t_0}^t i d t + v(t_0)$$

## 6.1 Capacitors (4)

- The energy,  $w$ , stored in the capacitor is


$$w = \frac{1}{2} C v^2$$

(หน่วย J)

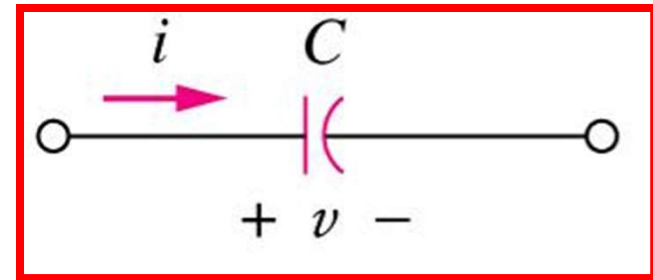


- A capacitor is
  - an **open circuit** to dc ( $dv/dt = 0$ ).
  - its voltage **cannot change abruptly**.




## 6.1 Capacitors (5)

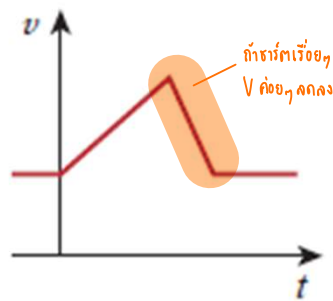

(a)

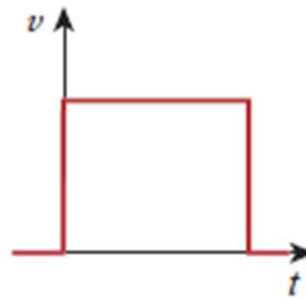

(b)

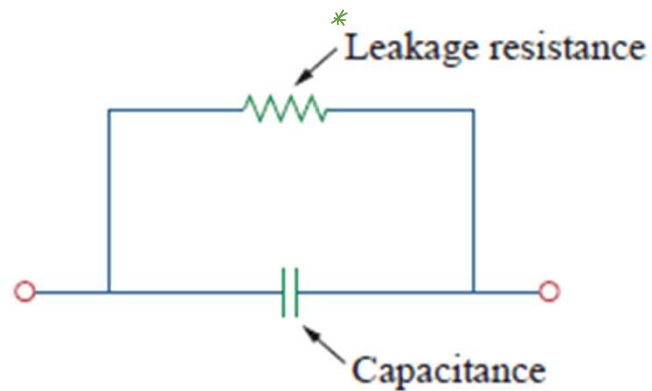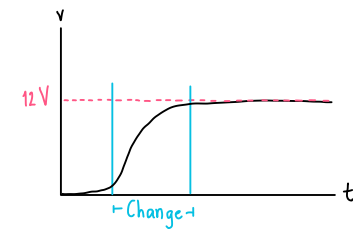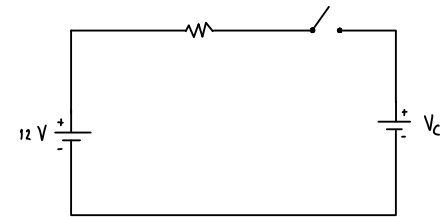



## 6.1 Capacitors (6)

- (a) Calculate the charge stored on a 3-pF capacitor with 20 V across it.
- (b) Find the energy stored in the capacitor.

### **Solution:**

- (a) Since  $q = Cv$ ,

$$q = 3 \times 10^{-12} \times 20 = 60 \text{ pC}$$

- (b) The energy stored is

$$w = \frac{1}{2}Cv^2 = \frac{1}{2} \times 3 \times 10^{-12} \times 400 = 600 \text{ pJ}$$








## 6.1 Capacitors (7)

The voltage across a  $5\text{-}\mu\text{F}$  capacitor is


$$v(t) = 10 \cos 6000t \text{ V}$$



Calculate the current through it.

**Solution:**

By definition, the current is

$$\begin{aligned} i(t) &= C \frac{dv}{dt} = 5 \times 10^{-6} \frac{d}{dt}(10 \cos 6000t) \\ &= -5 \times 10^{-6} \times 6000 \times 10 \sin 6000t = -0.3 \sin 6000t \text{ A} \end{aligned}$$




## 6.1 Capacitors (8)

Determine the voltage across a  $2\text{-}\mu\text{F}$  capacitor if the current through it is

$$i(t) = 6e^{-3000t} \text{ mA}$$

Assume that the initial capacitor voltage is zero.




### **Solution:**

Since  $v = \frac{1}{C} \int_0^t i \, dt + v(0)$  and  $v(0) = 0$ ,


$$\begin{aligned} v &= \frac{1}{2 \times 10^{-6}} \int_0^t 6e^{-3000t} \, dt \cdot 10^{-3} \\ &= \frac{3 \times 10^3}{-3000} e^{-3000t} \Big|_0^t = (1 - e^{-3000t}) \text{ V} \end{aligned}$$
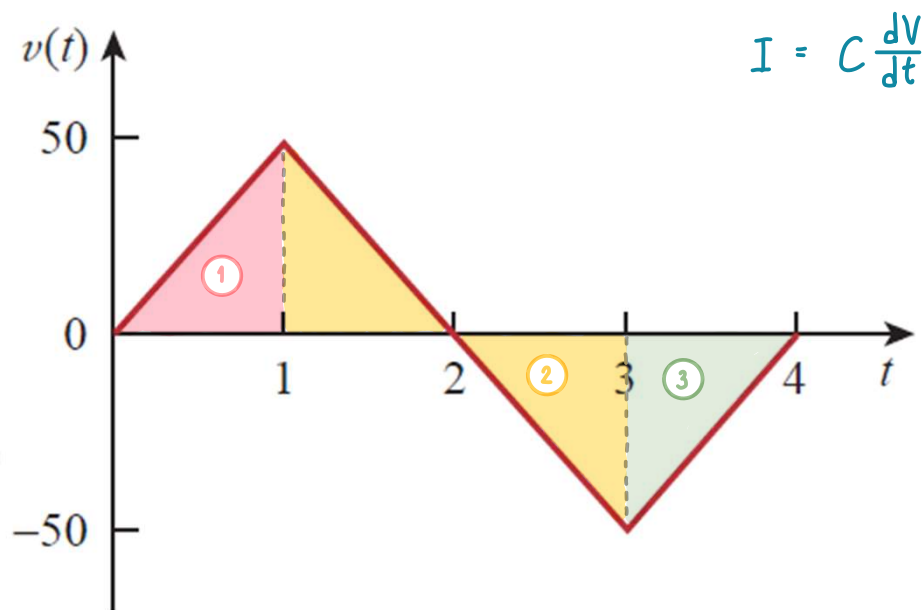
## 6.1 Capacitors (9)

Determine the current through a  $200\text{-}\mu\text{F}$  capacitor whose voltage is shown in Fig. 6.9.



## 6.1 Capacitors (10)

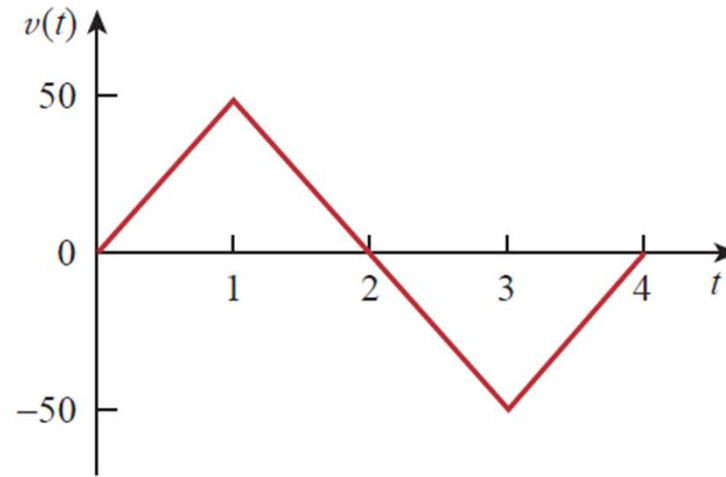

The voltage waveform can be described mathematically as

$$v(t) = \begin{cases} 50t \text{ V} & 0 < t < 1 \\ 100 - 50t \text{ V} & 1 < t < 3 \\ -200 + 50t \text{ V} & 3 < t < 4 \\ 0 & \text{otherwise} \end{cases}$$




## 6.1 Capacitors (11)

Since  $i = C dv/dt$  and  $C = 200 \mu\text{F}$ , we take the derivative of  $v$  to obtain

$$i(t) = 200 \times 10^{-6} \times \begin{cases} 50 & 0 < t < 1 \\ -50 & 1 < t < 3 \\ 50 & 3 < t < 4 \\ 0 & \text{otherwise} \end{cases}$$
$$= \begin{cases} 10 \text{ mA} & 0 < t < 1 \\ -10 \text{ mA} & 1 < t < 3 \\ 10 \text{ mA} & 3 < t < 4 \\ 0 & \text{otherwise} \end{cases}$$

Thus the current waveform is as shown in Fig. 6.10.

## 6.1 Capacitors (12)

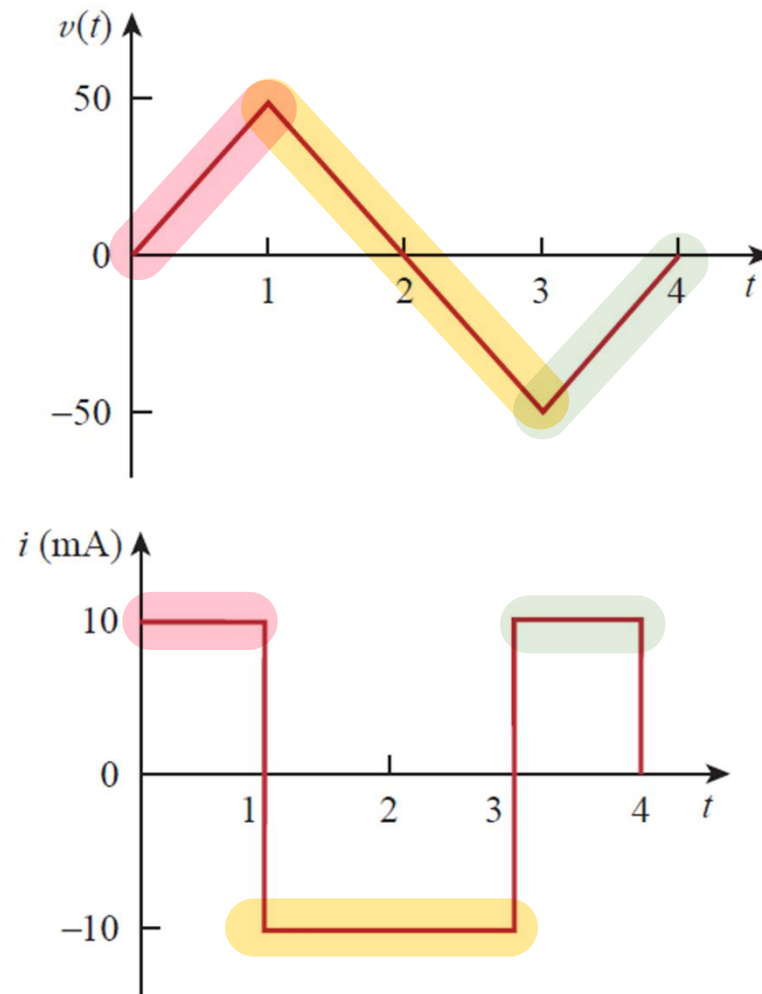

# 6.1 Capacitors (13)


## Example

An initially uncharged  $1 \times 10^{-3} \text{ F}$  capacitor has the current shown below across it.

Calculate the voltage across it at  $t = 2 \text{ ms}$  and  $t = 5 \text{ ms}$ .



$$\begin{aligned} i &= C \frac{dV}{dt} \\ C dV &= i dt \\ dt &= \frac{1}{C} i dt \\ V &= \frac{1}{C} \int i dt \end{aligned}$$

พื้นที่ใต้กราฟ

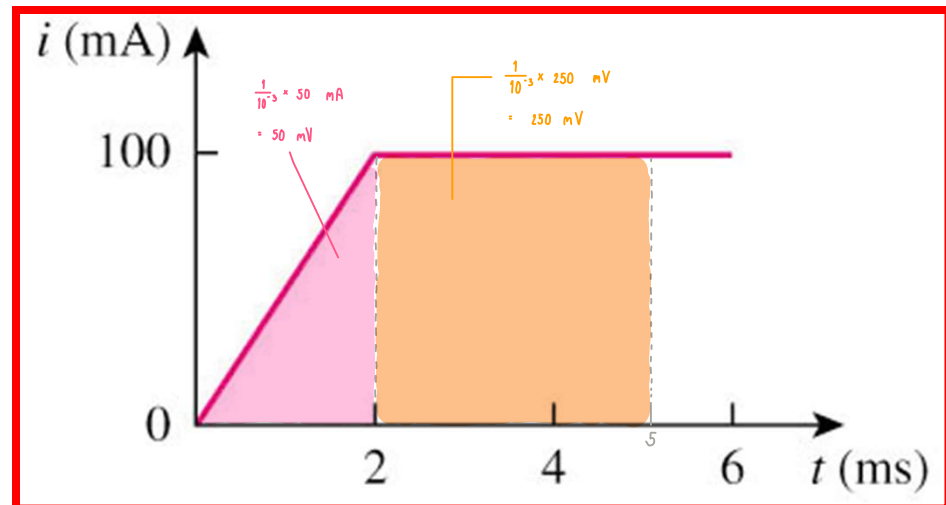

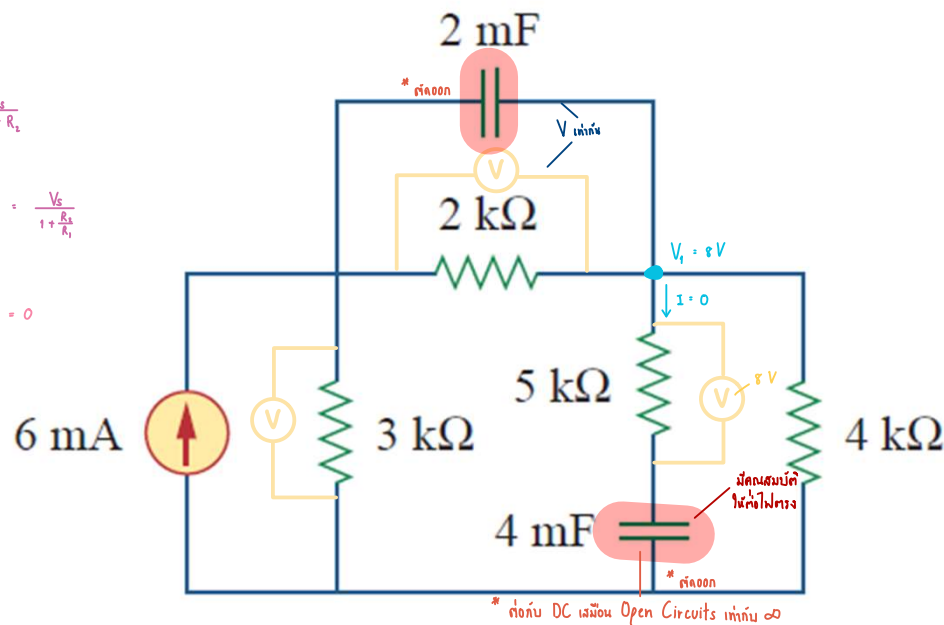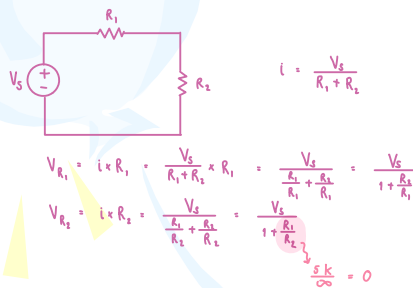
# 6.1 Capacitors (14)

Obtain the energy stored in each capacitor in Fig. 6.12(a) under dc conditions.



$$W = \frac{1}{2} CV^2$$


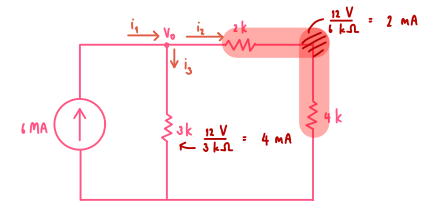


$$\begin{aligned}
 i_1 &= i_2 + i_3 \\
 6 \text{ mA} &= \frac{V_0}{4 \text{ k}} + \frac{V_0}{3 \text{ k}} \\
 36 &= V_0 + 2V_0 \\
 3V_0 &= 36 \\
 V_0 &= 12 \text{ V}
 \end{aligned}$$

# Resistor  $\propto$  Capacitor มีพลังงาน





## 6.1 Capacitors (15)

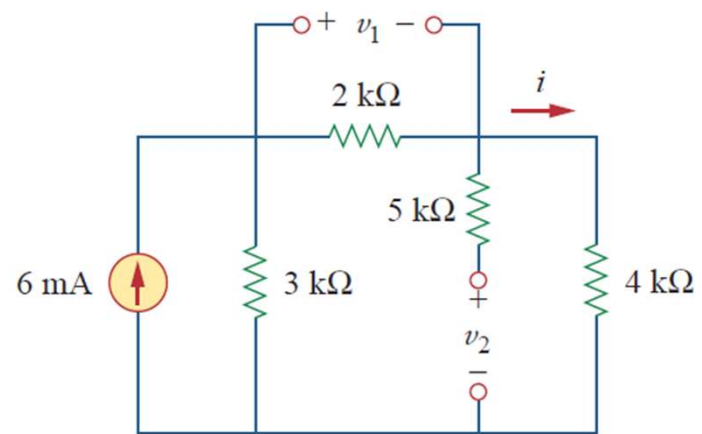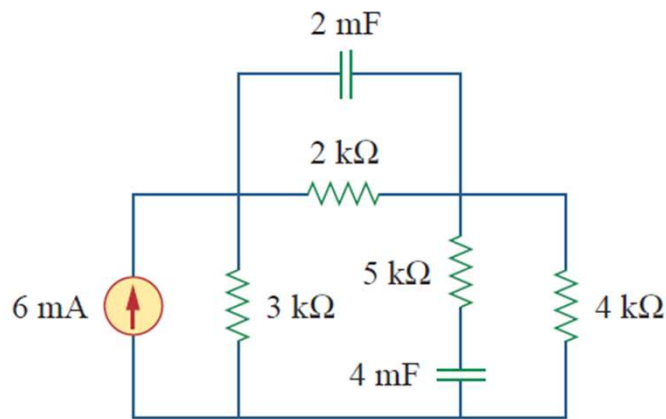

Under dc conditions, we replace each capacitor with an open circuit, as shown in Fig. 6.12(b). The current through the series combination of the 2-kΩ and 4-kΩ resistors is obtained by current division as

$$i = \frac{3}{3 + 2 + 4}(6 \text{ mA}) = 2 \text{ mA}$$

## 6.1 Capacitors (16)

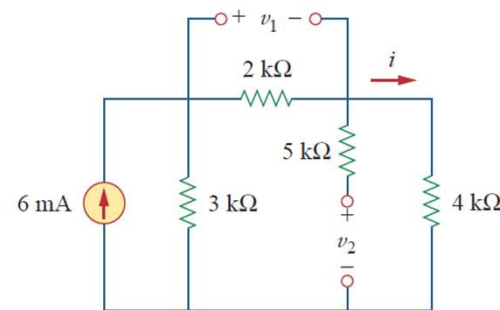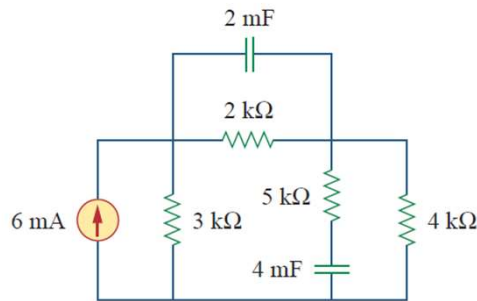

Hence, the voltages  $v_1$  and  $v_2$  across the capacitors are

$$v_1 = 2000i = 4 \text{ V} \quad v_2 = 4000i = 8 \text{ V}$$


and the energies stored in them are

$$w_1 = \frac{1}{2}C_1v_1^2 = \frac{1}{2}(2 \times 10^{-3})(4)^2 = 16 \text{ mJ}$$

$$w_2 = \frac{1}{2}C_2v_2^2 = \frac{1}{2}(4 \times 10^{-3})(8)^2 = 128 \text{ mJ}$$

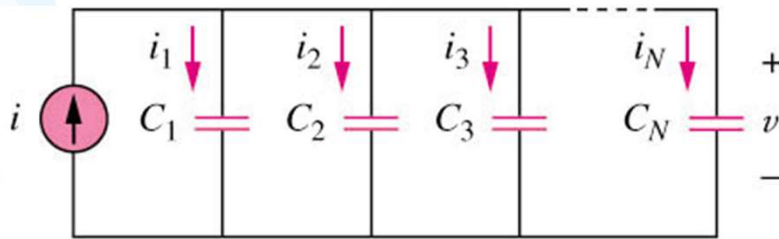
## 6.2 Series and Parallel Capacitors (1)

- The equivalent capacitance of  $N$  **parallel-connected** capacitors is the sum of the individual capacitances.



(a)


$$C_{eq} = C_1 + C_2 + \dots + C_N$$

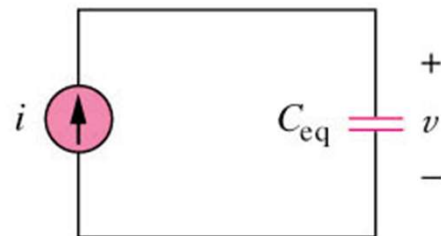

(b)

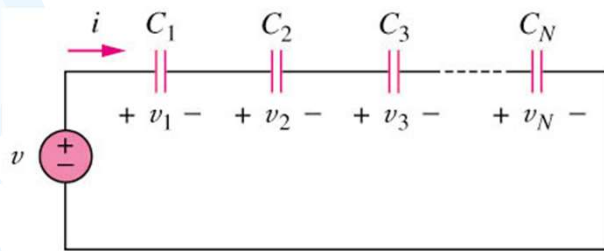
## 6.2 Series and Parallel Capacitors (2)

- The equivalent capacitance of  $N$  **series-connected** capacitors is the reciprocal of the sum of the reciprocals of the individual capacitances.



(a)

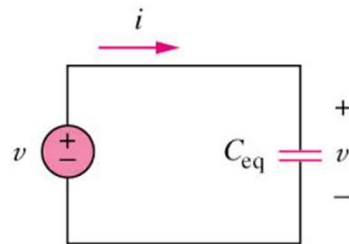
$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N}$$



(b)
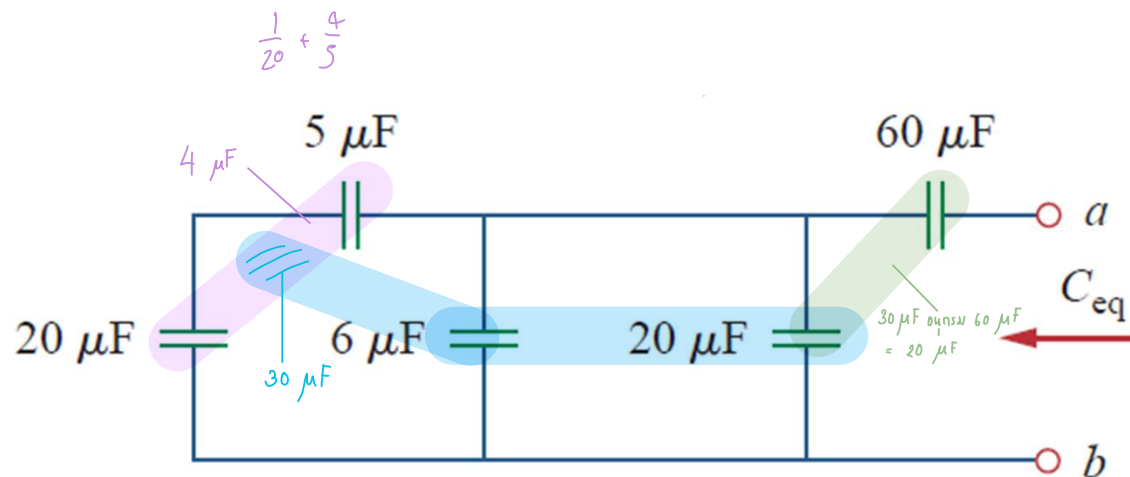
## 6.2 Series and Parallel Capacitors (4)


Find the equivalent capacitance seen between terminals  $a$  and  $b$  of the circuit in Fig. 6.16.



## 6.2 Series and Parallel Capacitors (5)
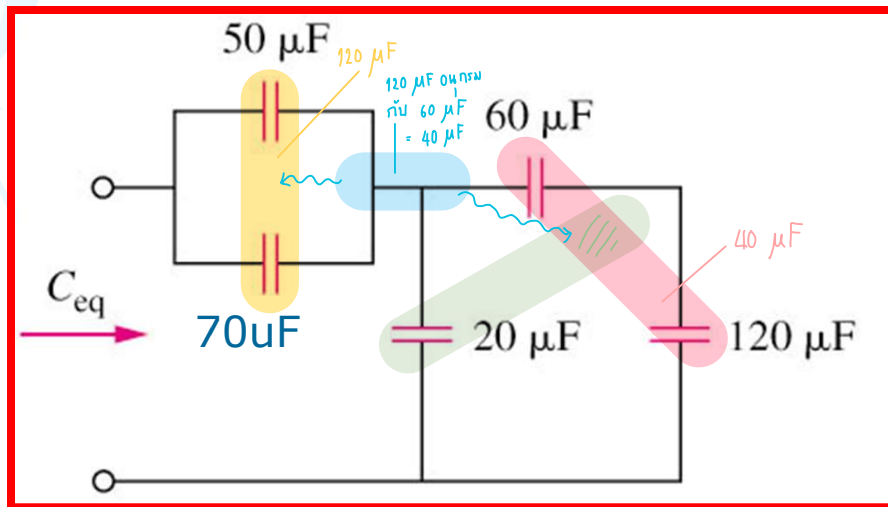
### Example 3

Find the equivalent capacitance seen at the terminals of the circuit in the circuit shown below:



**Answer:**

$$C_{eq} = \underline{40\ \mu\text{F}}$$

## 6.2 Series and Parallel Capacitors (6)


For the circuit in Fig. 6.18, find the voltage across each capacitor.

q.m!

$$q = CV$$

$$W = \frac{1}{2} CV^2$$

$$i = C \frac{dV}{dt}$$

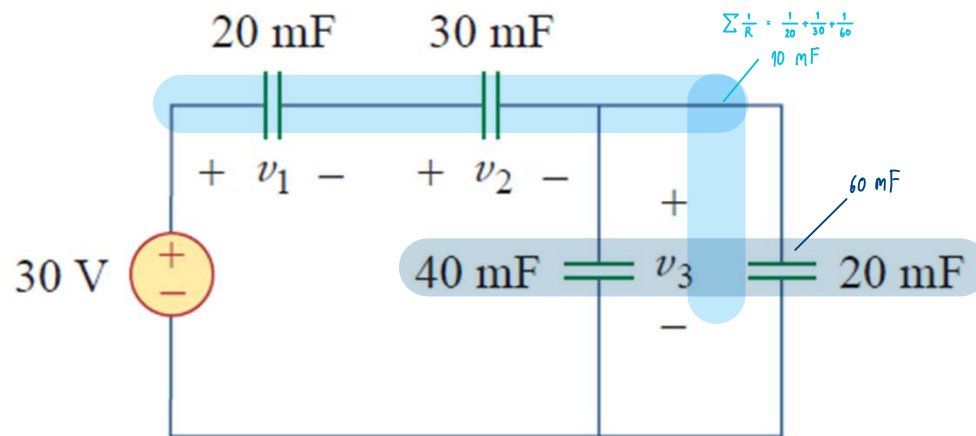

$$W = \frac{1}{2} (10 \text{ m})(30^2)$$

$$= 4.5 \text{ J}$$

$$q = (10 \text{ m})(30)$$

$$= 300 \text{ mC}$$

$$\therefore C_{eq} = 10 \text{ mF}$$

$$30 \text{ V} = V_1 + V_2 + V_3$$


$$= \frac{q}{C_1} + \frac{q}{C_2} + \frac{q}{C_3}$$

$$= \frac{300 \text{ mC}}{20 \text{ mF}} + \frac{300 \text{ mC}}{30 \text{ mF}} + \frac{300 \text{ mC}}{60 \text{ mF}} = 15 \text{ V} + 10 \text{ V} + 5 \text{ V} = 30 \text{ V}$$

## 6.2 Series and Parallel Capacitors (7)
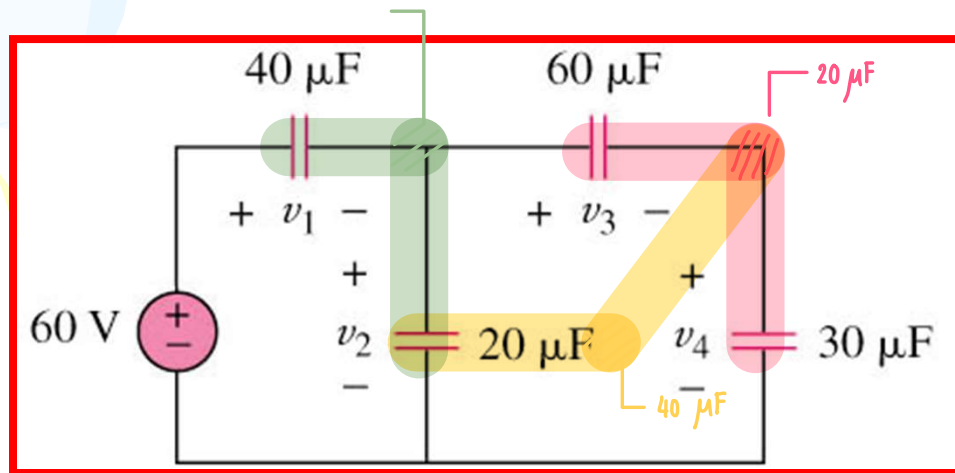
### Example 4

Find the voltage across each of the capacitors in the circuit shown below:



**Answer:**

$$v_1 = 30V$$

$$v_2 = 30V$$

$$v_3 = 10V$$


$$v_4 = 20V$$

$$\begin{aligned} Q &= CV_2 \\ &= 20 \mu F \times 30V \\ &= 600 \mu C \\ V_3 &= \frac{600 \mu C}{60} \\ &= 10 V \\ V_4 &= \frac{600 \mu C}{30} \\ &= 20 V \end{aligned}$$


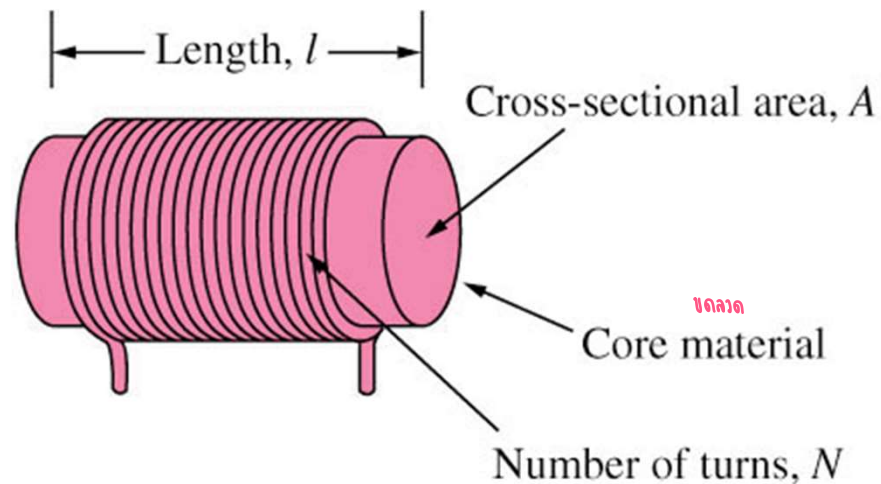
## 6.3 Inductors (1)

- An inductor is a passive element designed to store energy in its magnetic field.



- An inductor consists of a coil of conducting wire.

## 6.3 Inductors (2)

- Inductance is the property whereby an inductor exhibits opposition to the change of current flowing through it, measured in henrys (H).

$$v = L \frac{di}{dt} \quad \text{and} \quad L = \frac{N^2 \mu A}{l}$$

การเปลี่ยนแปลงของกระแสไฟฟ้า  
เทียบกับเวลา

หน่วย

- The unit of inductors is Henry (H), mH ( $10^{-3}$ ) and  $\mu\text{H}$  ( $10^{-6}$ ).

## 6.3 Inductors (3)

- The current-voltage relationship of an inductor:


$$i = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0)$$

\* กระแสตรง (DC) : เป็น short circuit



- The power stored by an inductor:

$$w = \frac{1}{2} L i^2$$

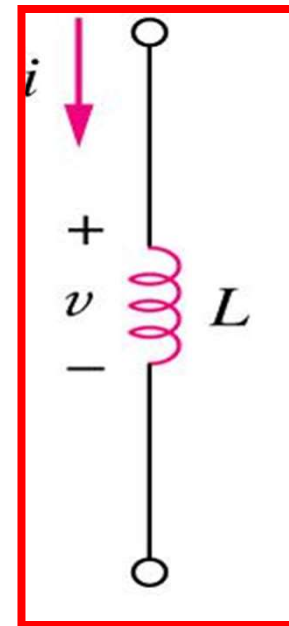


- An inductor acts like a short circuit to dc ( $di/dt = 0$ ) and its current **cannot change abruptly**.

## Inductors (3)




(a)

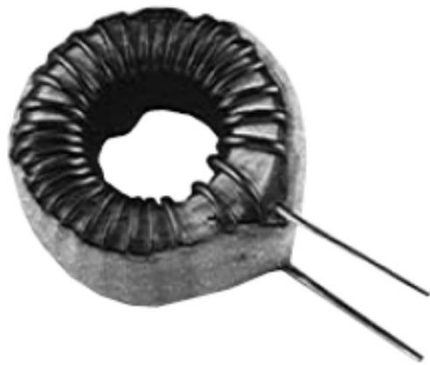


(b)




(c)

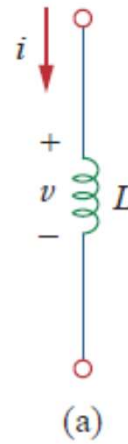

(a)

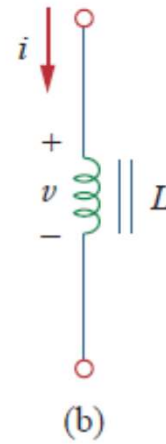

(b)

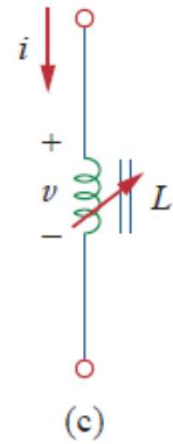

(c)




## 6.3 Inductors (4)

The current through a 0.1-H inductor is  $i(t) = 10te^{-5t}$  A. Find the voltage across the inductor and the energy stored in it.
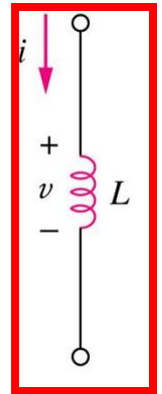
### Solution:

Since  $v = L di/dt$  and  $L = 0.1$  H,

$$v = 0.1 \frac{d}{dt} (10te^{-5t}) = e^{-5t} + t(-5)e^{-5t} = e^{-5t}(1 - 5t) \text{ V}$$



The energy stored is

$$w = \frac{1}{2} Li^2 = \frac{1}{2} (0.1) 100t^2 e^{-10t} = 5t^2 e^{-10t} \text{ J}$$

## 6.3 Inductors (5)

Find the current through a 5-H inductor if the voltage across it is


$$v(t) = \begin{cases} 30t^2, & t > 0 \\ 0, & t < 0 \end{cases}$$



Also, find the energy stored at  $t = 5$  s. Assume  $i(v) > 0$ .

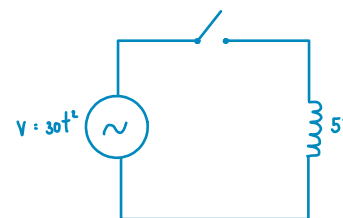**Solution:**

Since  $i = \frac{1}{L} \int_{t_0}^t v(t) dt + \underbrace{i(t_0)}_{t \text{ เริ่มที่}}$  and  $L = 5$  H,

$$i = \frac{1}{5} \int_0^t 30t^2 dt + 0 = 6 \times \frac{t^3}{3} = 2t^3 \text{ A}$$



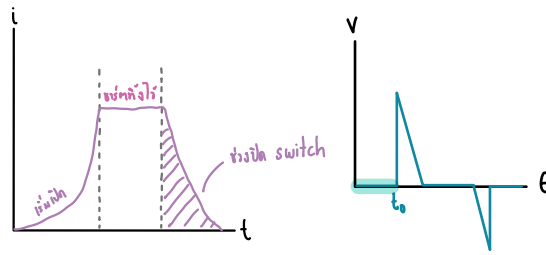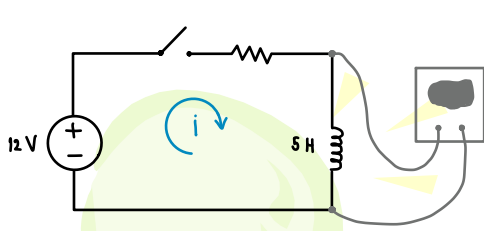

## 6.3 Inductors (6)

The power  $p = vi = 60t^5$ , and the energy stored is then

$$w = \int p \, dt = \int_0^5 60t^5 \, dt = 60 \frac{t^6}{6} \Big|_0^5 = 156.25 \text{ kJ}$$

Alternatively, we can obtain the energy stored using Eq. (6.24), by writing

$$w|_0^5 = \frac{1}{2}Li^2(5) - \frac{1}{2}Li^2(0) = \frac{1}{2}(5)(2 \times 5^3)^2 - 0 = 156.25 \text{ kJ}$$

as obtained before.

## 6.3 Inductors (7)

### Example 5

The terminal voltage of a 2-H inductor is

$$v = 10(1-t) \text{ V}$$

Find the current flowing through it at  $t = 4 \text{ s}$  and the energy stored in it within  $0 < t < 4 \text{ s}$ .


Assume  $i(0) = 2 \text{ A}$ .

$$\begin{aligned} i &= \frac{1}{L} \int_{t_0}^t v \, dt + i_0 \\ &= \frac{1}{2} \int_0^4 (10(1-t)) \, dt + 2 \\ &= \frac{1}{2} \left( 10t - 5t^2 \right) \Big|_0^4 + 2 \\ &= \frac{1}{2} (40 - 80) + 2 \\ &= -20 + 2 = -18 \end{aligned}$$

**Answer:**

$$i(4\text{s}) = -18\text{A}$$

$$w(4\text{s}) = 320\text{J}$$

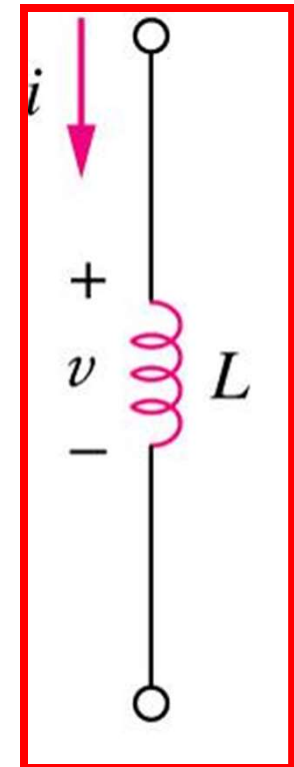


$$\begin{aligned} W &= \frac{1}{2} Li^2 \Big|_{t=4} - \frac{1}{2} Li^2 \Big|_{t=0} \\ &= \frac{1}{2} \times 2 \times (-18)^2 - \frac{1}{2} \times 2 \times 2^2 \\ &= 324 - 4 = 320 \end{aligned}$$


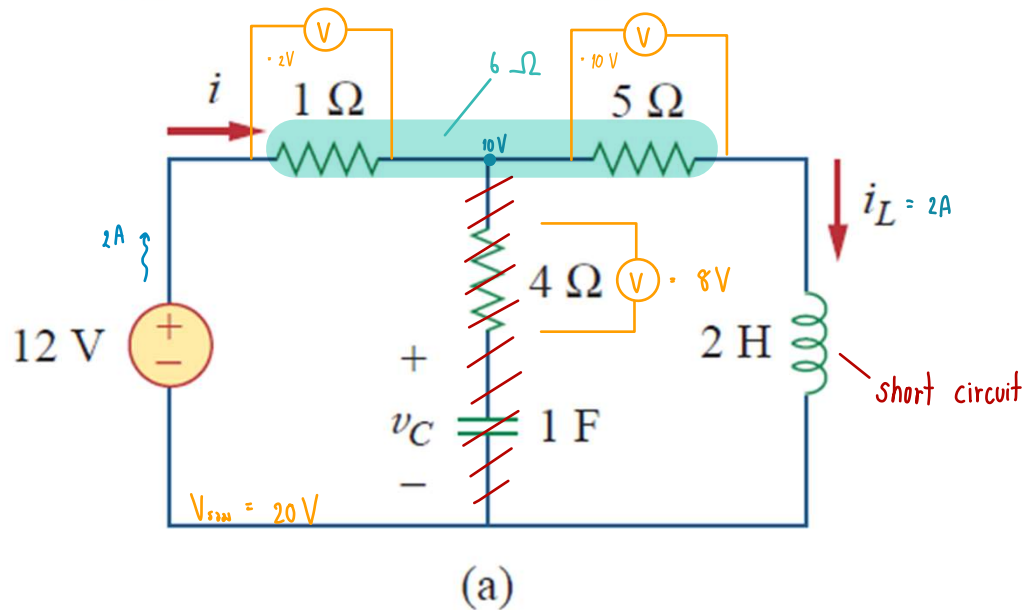
## 6.3 Inductors (8)



Consider the circuit in Fig. 6.27(a). Under dc conditions, find: (a)  $i$ ,  $v_C$ , and  $i_L$ , (b) the energy stored in the capacitor and inductor.



## 6.3 Inductors (9)
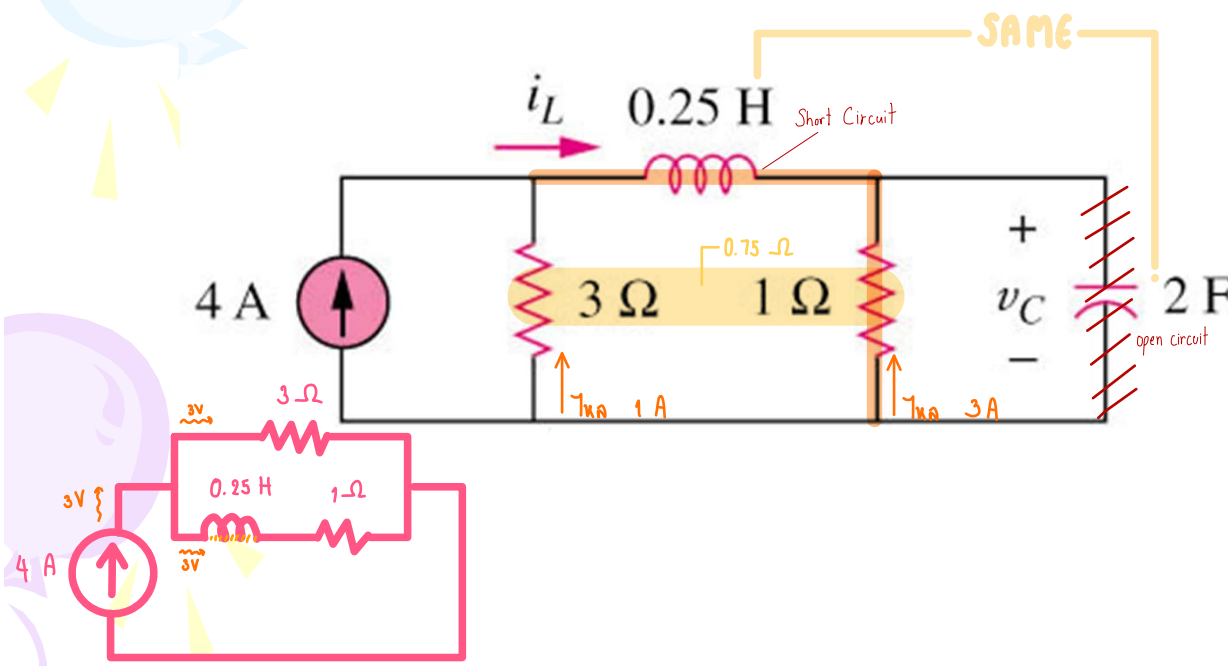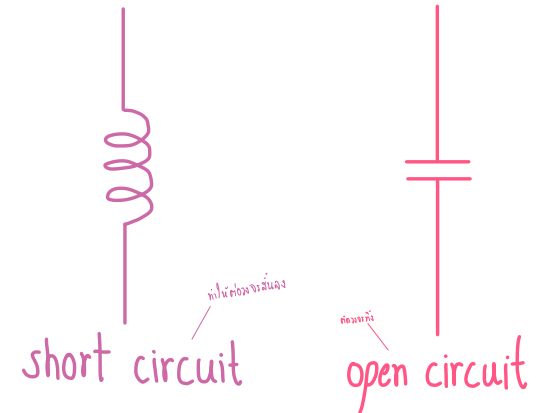
### Example 6

Determine  $v_C$ ,  $i_L$ , and the energy stored in the capacitor and inductor in the circuit of circuit shown below under dc conditions.



**Answer:**

$$i_L = 3A$$


$$v_C = 3V$$

$$w_L = 1.125J$$


$$w_C = 9J$$
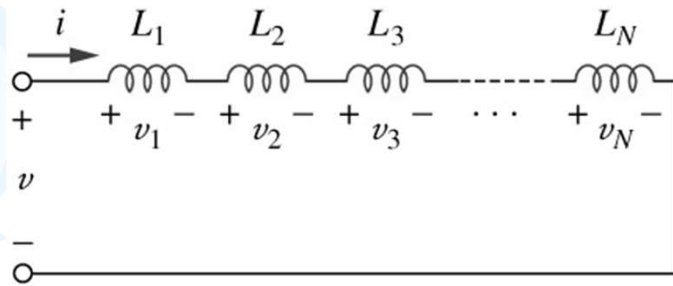
## 6.4 Series and Parallel Inductors (1)

- The equivalent inductance of **series-connected** inductors is the sum of the individual inductances.



(a)

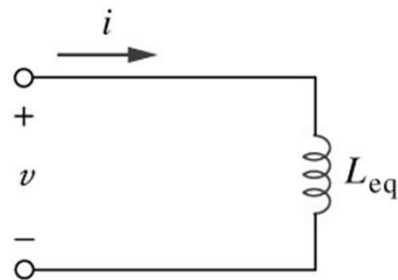


(b)


$$L_{eq} = L_1 + L_2 + \dots + L_N$$
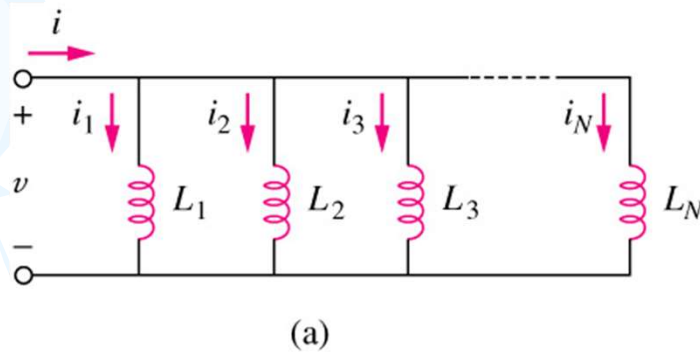
## 6.4 Series and Parallel Inductors (2)

- The equivalent capacitance of **parallel** inductors is the reciprocal of the sum of the reciprocals of the individual inductances.



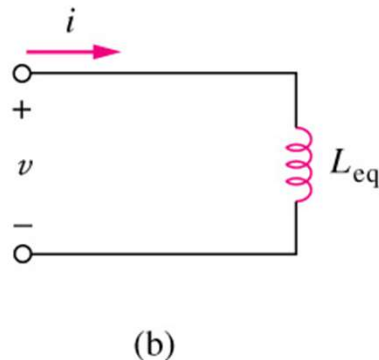
$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N}$$


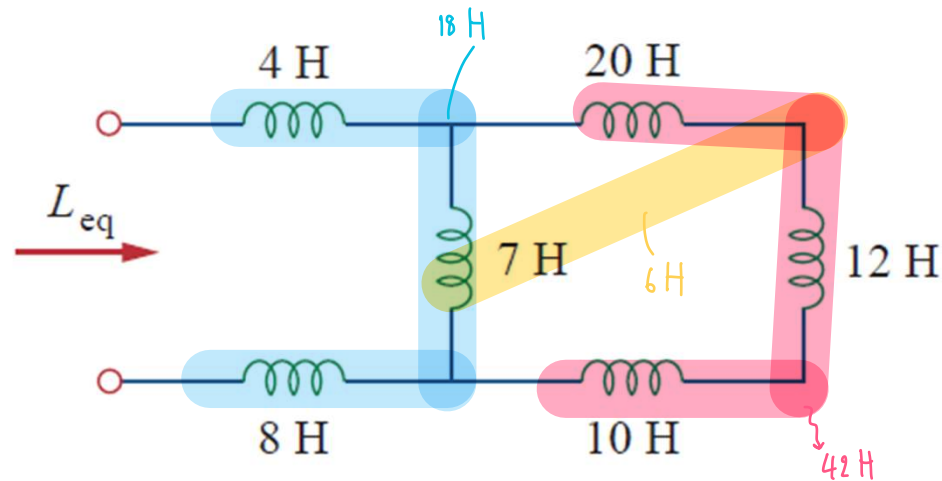
## 6.4 Series and Parallel Capacitors (3)


Find the equivalent inductance of the circuit



## 6.4 Series and Parallel Capacitors (3)
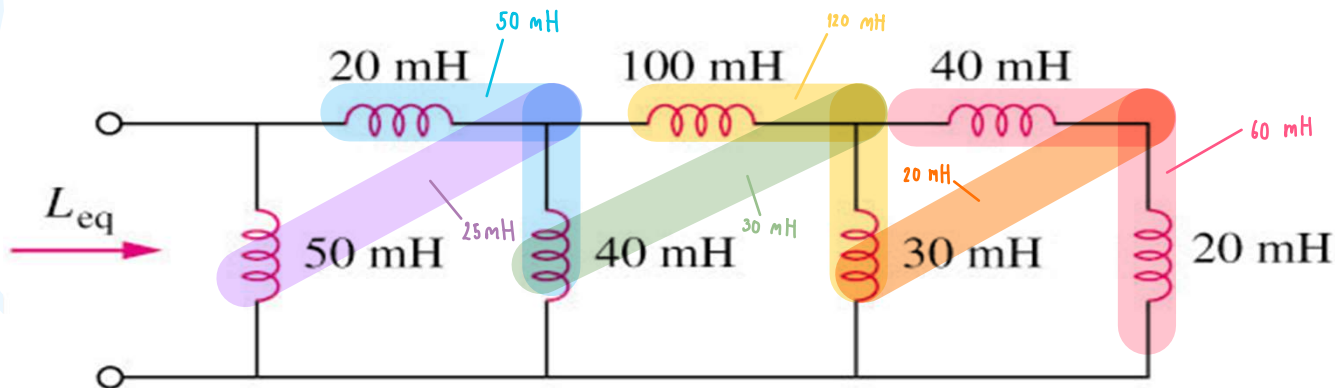
### Example 7

Calculate the equivalent inductance for the inductive ladder network in the circuit shown below:






**Answer:**

$$L_{eq} = \underline{25\text{mH}}$$

## 6.4 Series and Parallel Capacitors (4)

- Current and voltage relationship for R, L, C

Circuit element	Units	Voltage	Current	Power
 <b>Resistance</b>	ohms ( $\Omega$ )	$v = Ri$ (Ohm's law)	$i = \frac{v}{R}$	$p = vi = i^2 R$
 <b>Inductance</b>	henries (H)	$v = L \frac{di}{dt}$	$i = \frac{1}{L} \int v dt + k_1$	$p = vi = Li \frac{di}{dt}$
 <b>Capacitance</b>	farads (F)	$v = \frac{1}{C} \int i dt + k_2$	$i = C \frac{dv}{dt}$	$p = vi = Cv \frac{dv}{dt}$