



Fundamentals of Electric Circuits


Chapter 2

Basic Laws

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Basic Laws - Chapter 2

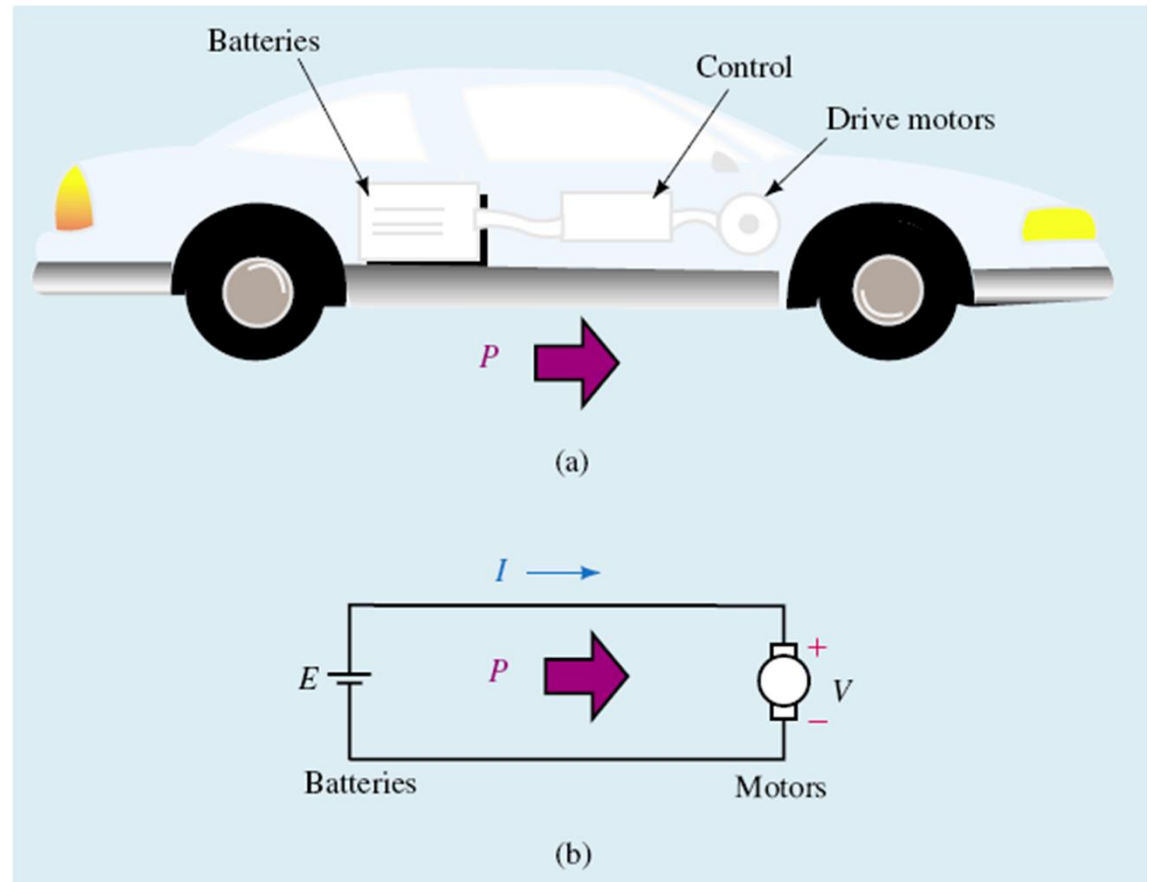- 2.1 Ohm's Law.
- 2.2 Nodes, Branches, and Loops.
- 2.3 Kirchhoff's Laws.
- 2.4 Series Resistors and Voltage Division.
- 2.5 Parallel Resistors and Current Division.
- 2.6 Wye-Delta Transformations.




2.1 Ohms Law (1)


- Ohm's law states that the voltage across a resistor is directly proportional to the current I flowing through the resistor.
- Mathematical expression for Ohm's Law is as follows:

$$v = iR$$

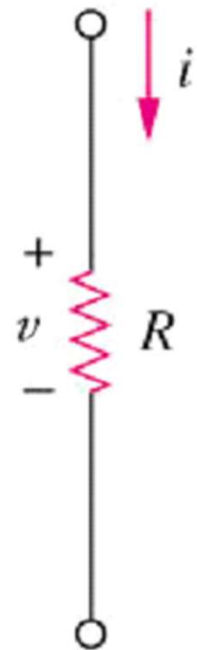
- Two extreme possible values of R :
0 (zero) and ∞ (**infinite**) are related with two basic circuit concepts: **short circuit** and **open circuit**.




Linear and nonlinear resistance

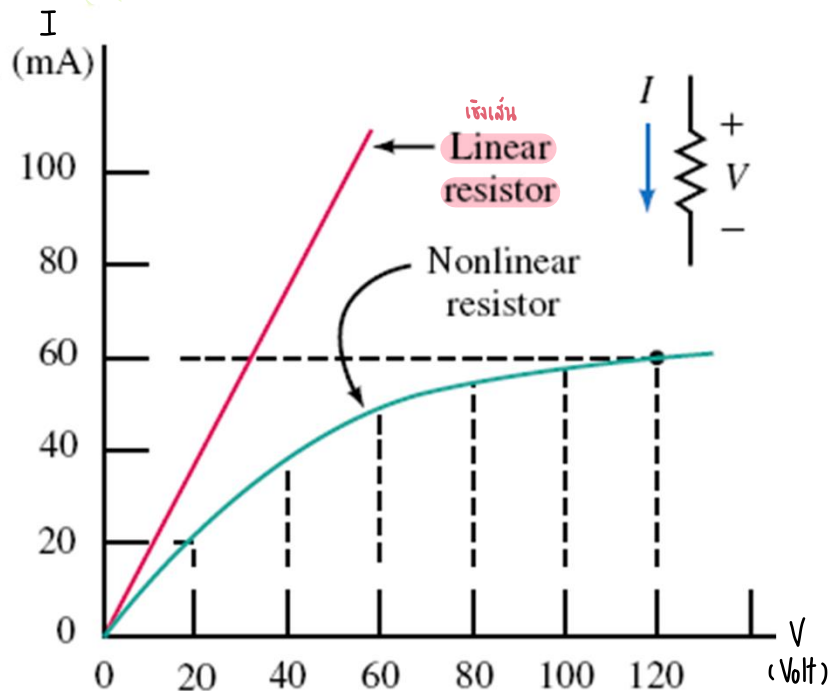

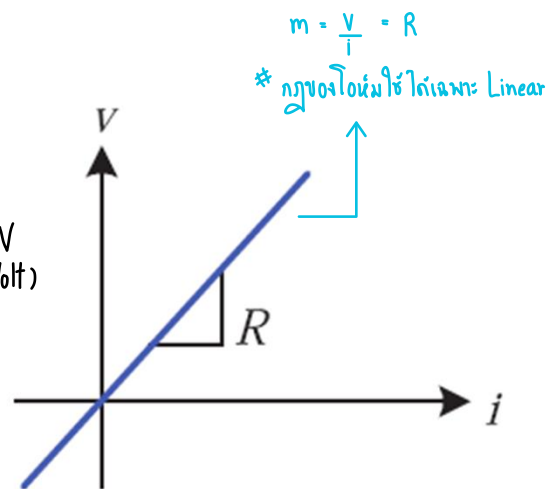Linear and nonlinear resistance characteristics.




Linear
(Ohm's Law Applies)

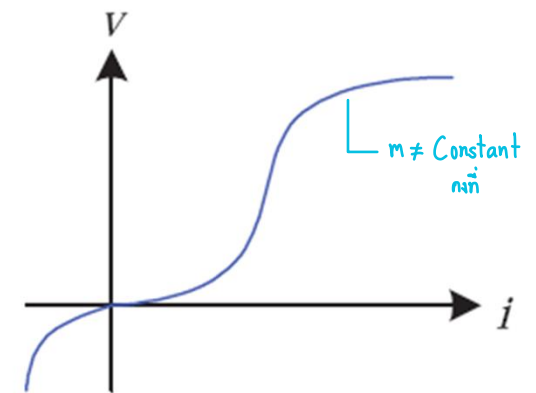


Nonlinear
(Ohm's Law Does Not Apply)

Short and open circuit

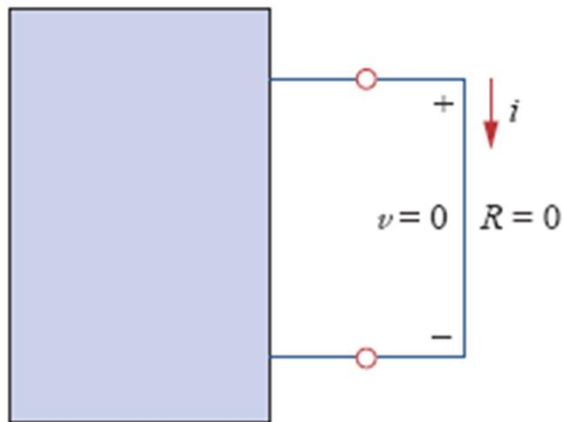A **short circuit** is a circuit element with resistance approaching zero.





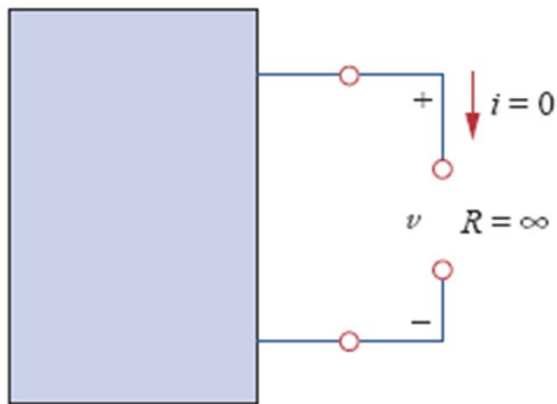An **open circuit** is a circuit element with resistance approaching infinity.




(b)

* Low Voltage < 1 kV.

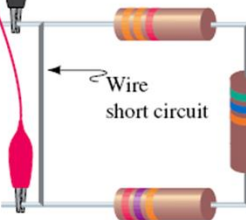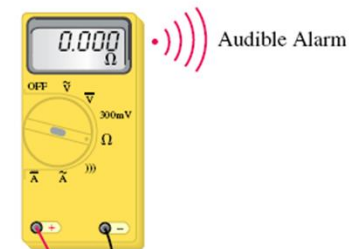

(a) Short circuit

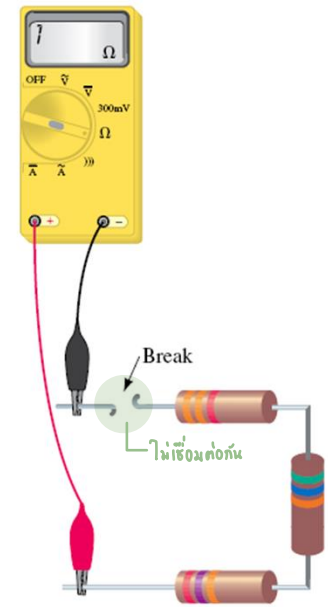

(b) Open circuit



2.1 Ohms Law (2)

- Conductance is the ability of an element to conduct electric current; it is the ^{ส่วนกลับ}reciprocal of resistance R and is measured in **mhos** or **siemens**.


$$G = \frac{1}{R} = \frac{i}{v}$$

- The power dissipated by a resistor: ^{$V = IR$}

$$\boxed{p = vi} = i^2 R = \frac{v^2}{R} ; I = \frac{V}{R}$$

Example

$$V = IR$$

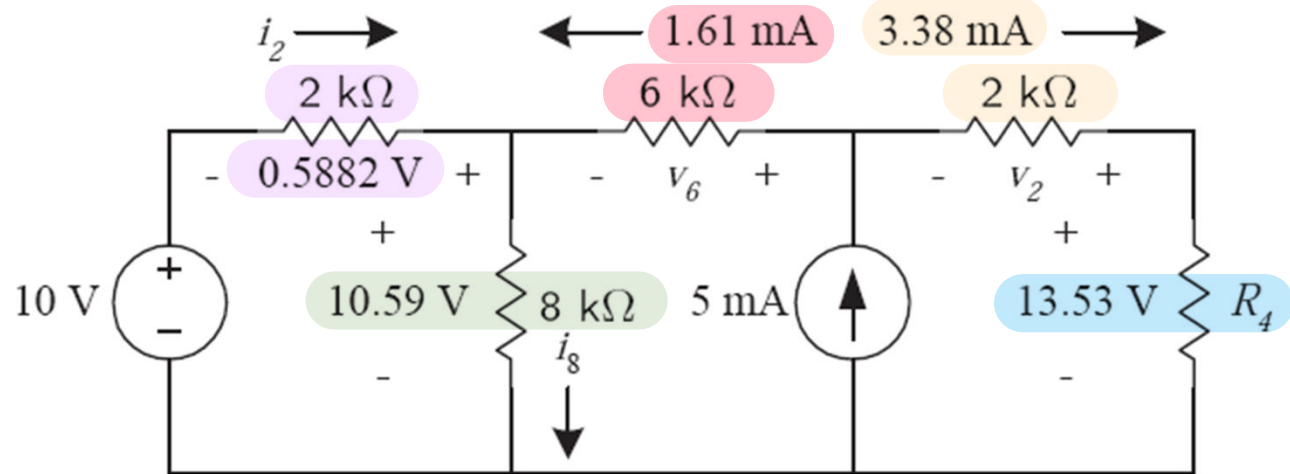

$$i_2 = 0.5882 \text{ V} / 2 \text{ k}\Omega = 0.000241 \text{ A} = 0.241 \text{ mA} = 241.1 \mu\text{A}$$

$$v_6 = 1.61 \times 10^{-3} \cdot 6 \times 10^3 = 9.66 \text{ V}$$

$$R_4 = 13.53 \text{ V} / 3.38 \text{ mA} = 4.003 \text{ k}\Omega$$

$$v_2 = 3.38 \times 10^{-3} \cdot 2 \times 10^3 = 6.76 \text{ V}$$

$$i_8 = 10.59 \text{ V} / 8 \text{ k}\Omega = 1.324 \text{ mA}$$

Conductance and resistivities

TABLE 2.1

Resistivities of common materials.

Material	Resistivity ($\Omega \cdot m$)	Usage
Silver	1.64×10^{-8}	Conductor
Copper	1.72×10^{-8}	Conductor
Aluminum	2.8×10^{-8}	Conductor
Gold	2.45×10^{-8}	Conductor
Carbon	4×10^{-5}	Semiconductor
Germanium	47×10^{-2}	Semiconductor
Silicon	6.4×10^2	Semiconductor
Paper	10^{10}	Insulator
Mica	5×10^{11}	Insulator
Glass	10^{12}	Insulator
Teflon	3×10^{12}	Insulator

* ฉนวนไฟฟ้า




ค่าความต้านทานไฟฟ้า

ค่าไฟฟ้าผก

ค่าไฟฟ้า

ทั้งค่าไฟฟ้า

ไม่ค่าไฟฟ้า

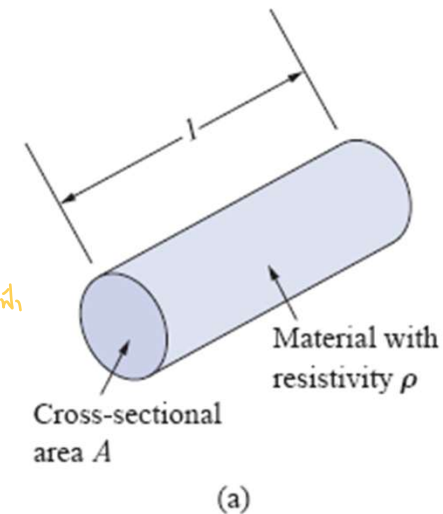

$$R = \rho \frac{L}{A}$$


Resistivity
ค่าความต้านทานต่อหน่วยพื้นที่

$$R = \frac{L}{\sigma A}$$

* ความหนาแน่นพื้นที่นำไฟฟ้า : นำไฟฟ้าได้

Heat produced by Current

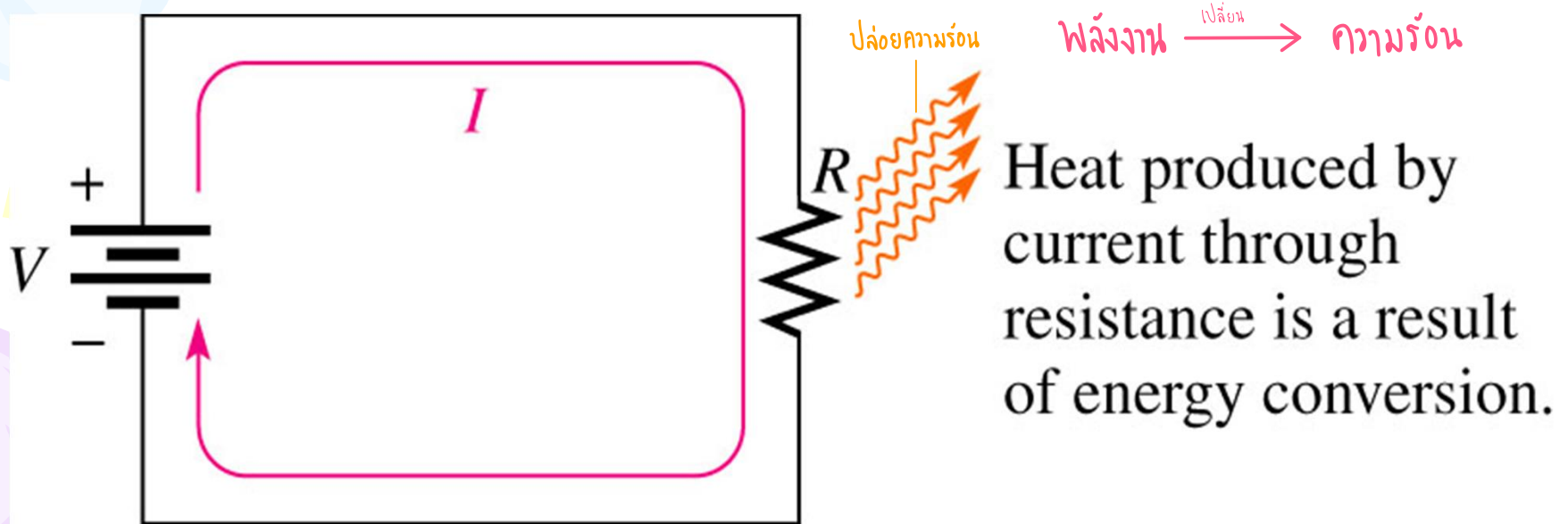
- When there is current through resistance, the collisions of the electrons produce heat, as a result of the conversion of electrical energy.




Resistor Power Rating

$$P = VI = I^2 R = \frac{V^2}{R}$$

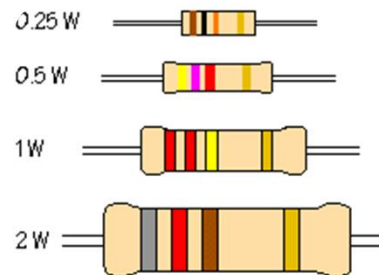Resistor power rating is not related to ohmic value (resistance) but rather is determined by the physical composition, size and shape of the resistor.




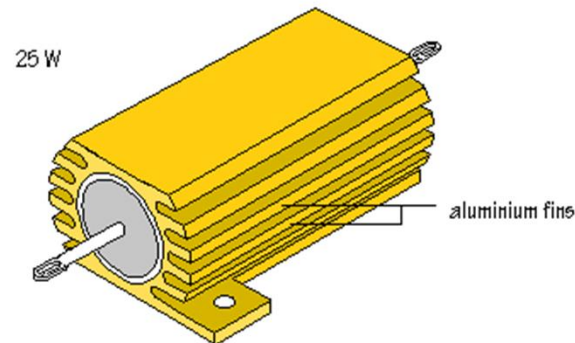* หมายเหตุ! : $W_{\text{minum}} \times 2 = W_{\text{จริง}}$




Resistor Power Rating

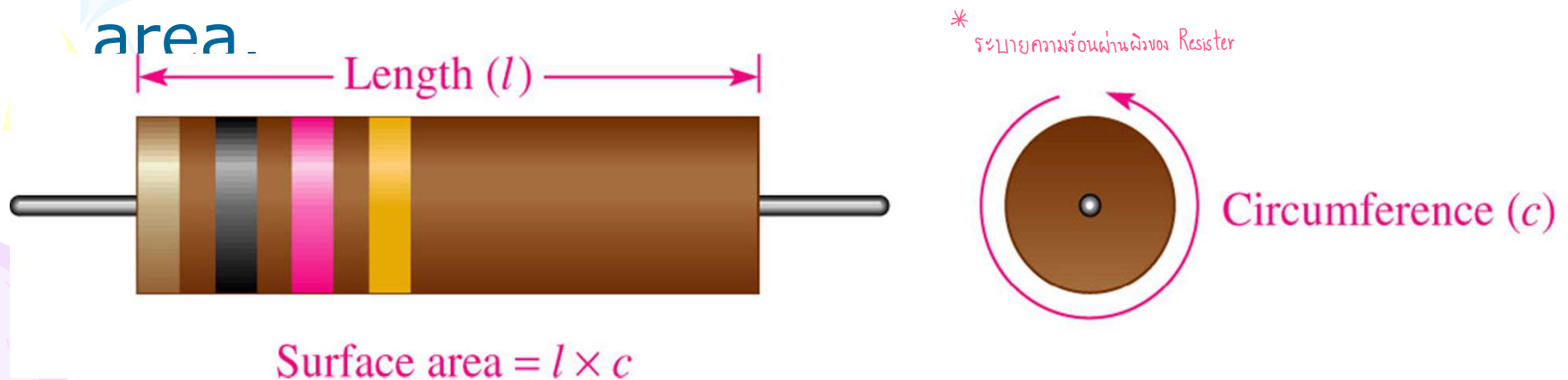- Power rating of a resistor is the maximum amount of power that a resistor can dissipate without being damaged by excessive heat buildup.
- Power rating is directly related to surface area.



Metal-film Resistors

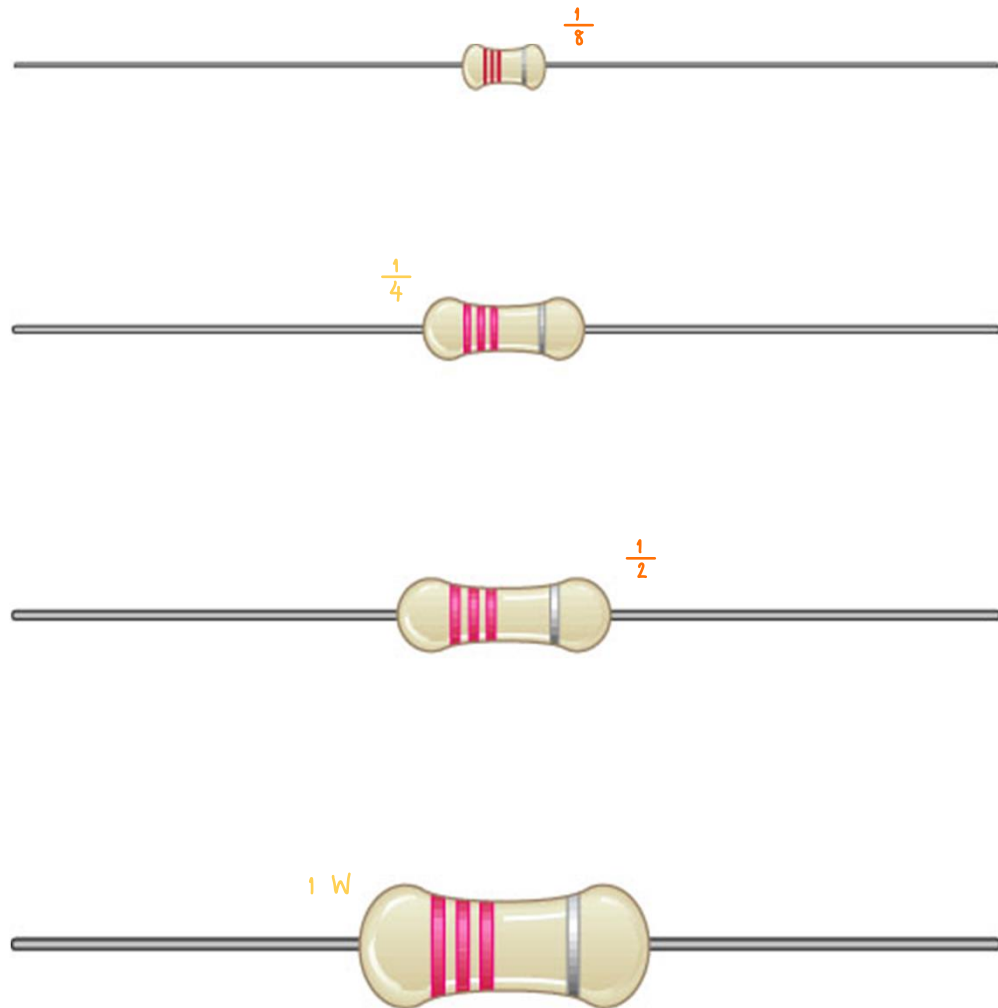Metal-film resistors have standard power ratings of $\frac{1}{8}$ W, $\frac{1}{4}$ W, $\frac{1}{2}$ W, and 1 W.






Selecting the Proper Power Rating

- A resistor used in a circuit must have a power rating in excess of what it will have to handle.
- Ideally, a rating that is approximately twice the actual power should be used when possible.


Resistor Failures

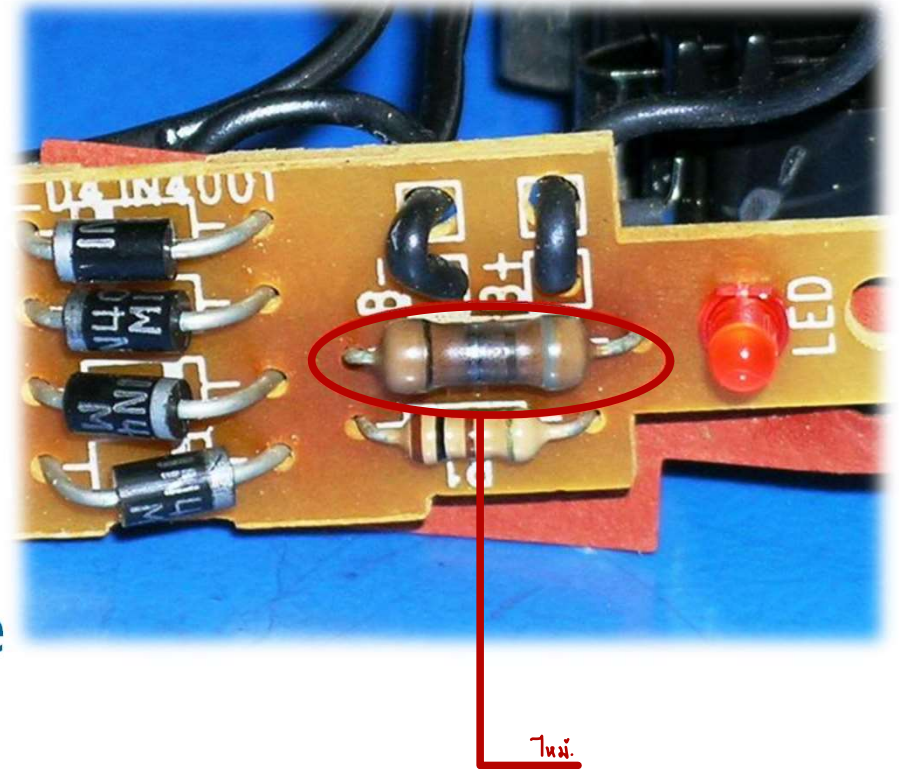- When excessive power is applied to a resistor, the resistor will overheat.
- The resistor will burn open, or its resistance value will be greatly altered.
- Overheated resistors may be charred, or the surface color may change.
- Resistors suspected of being damaged should be removed from the circuit and checked with an ohmmeter.



Energy Conversion and Voltage Drop in Resistance

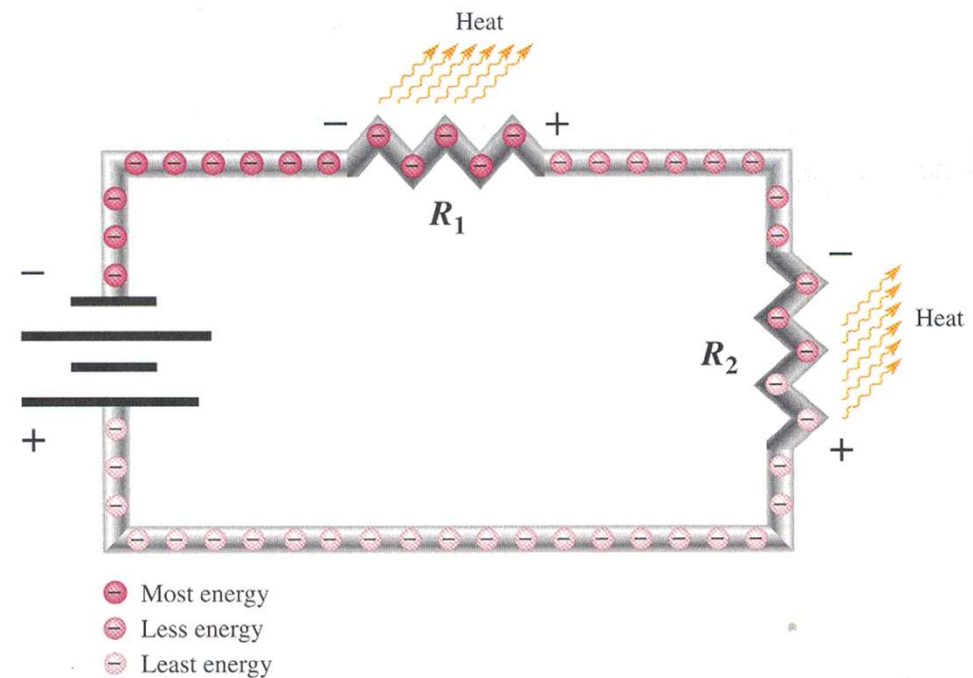- As electrons flow through resistors, some of their energy is given up as heat.
- The same number of electrons entering a resistor will exit it, only their energy will be less, so the voltage exiting a resistor is less than the voltage entering the resistor.





2.2 Nodes, Branches and Loops (1)

- A **branch** represents a single element such as a voltage source or a resistor. อุปกรณ์ไฟฟ้าที่อยู่ในวงจร : นับว่ากิ่งตัว
- A **node** is the point of connection between two or more branches. ตัวเชื่อมจุด
- A **loop** is any closed path in a circuit. ส่วน(จุด)ที่ทำให้วงจรปิด
- **Network** = interconnection of elements or devices
- **Circuit** = a network with closed paths
- A network with b branches, n nodes, and l independent loops will satisfy the fundamental theorem of network topology:

$$b = l + n - 1$$

2.2 Nodes, Branches and Loops (2)

Example 1

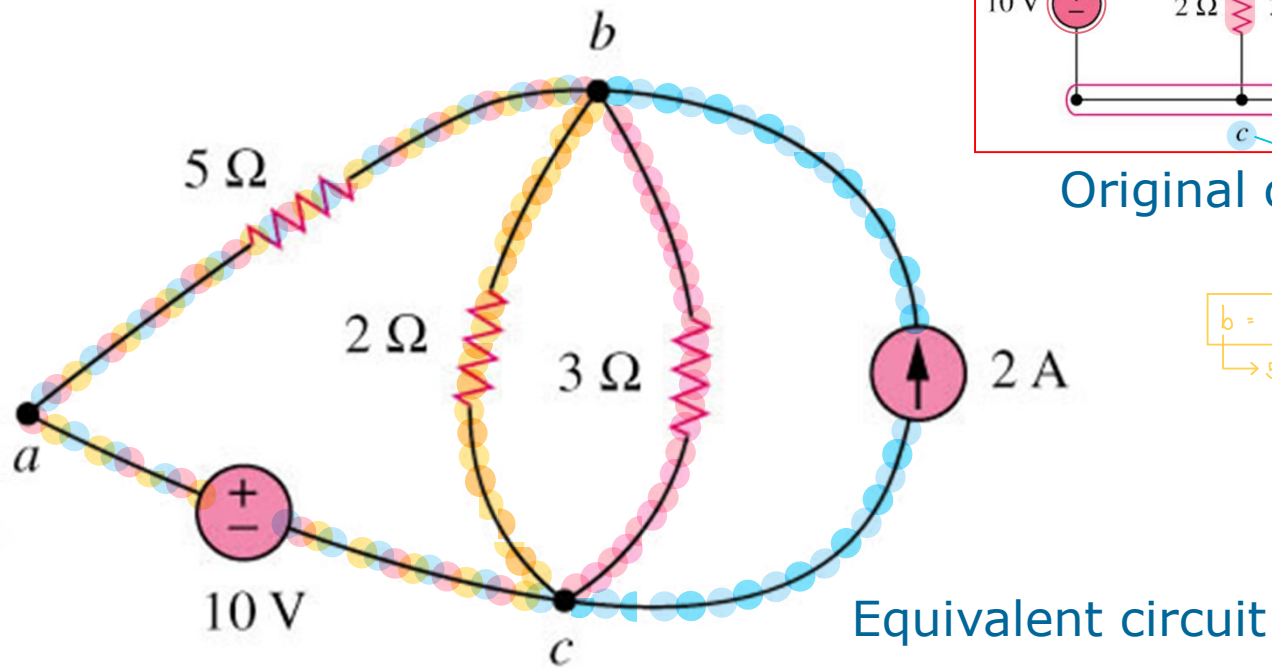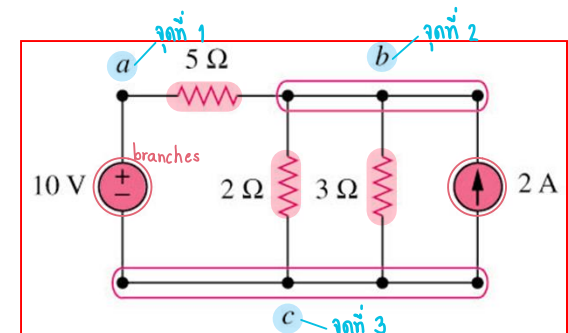


$$b = l + n - 1$$

$$\rightarrow 5 = 3 + 3 - 1$$

How many branches, nodes and loops are there?

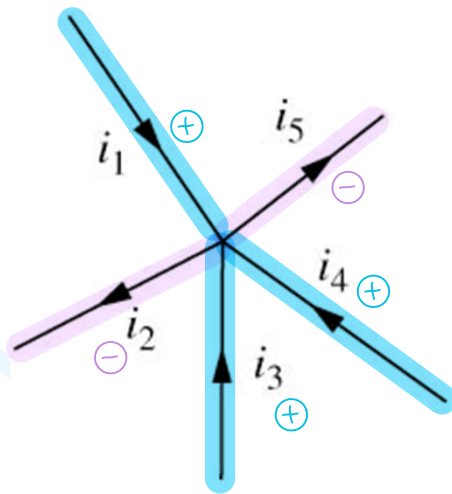
2.3 Kirchhoff's Laws (1)

- Kirchhoff's current law (KCL) states that the algebraic sum of currents entering a node (or a closed boundary) is zero.



Mathematically,


$$\sum_{n=1}^N i_n = 0$$

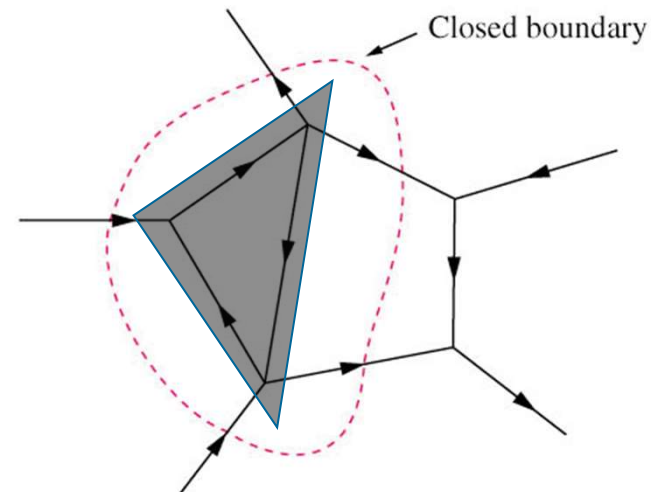

2.3 Kirchhoff's Laws (2)

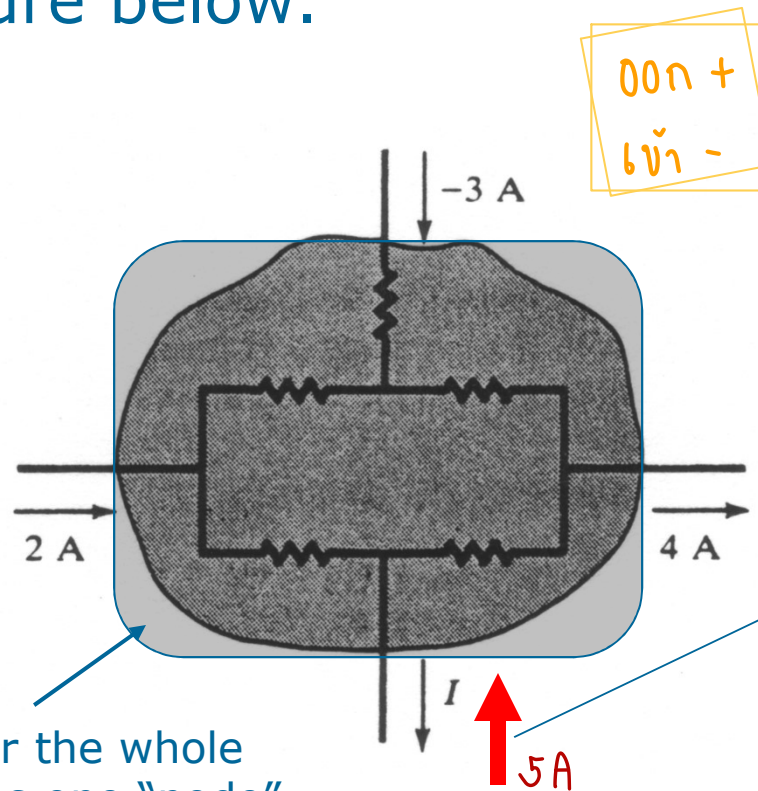Example 4

- Determine the current I for the circuit shown in the figure below.



$$I + 4 - (-3) - 2 = 0$$


$$\Rightarrow I = -5\text{ A}$$

This indicates that the actual current for I is flowing in the opposite direction.

We can consider the whole enclosed area as one "node".

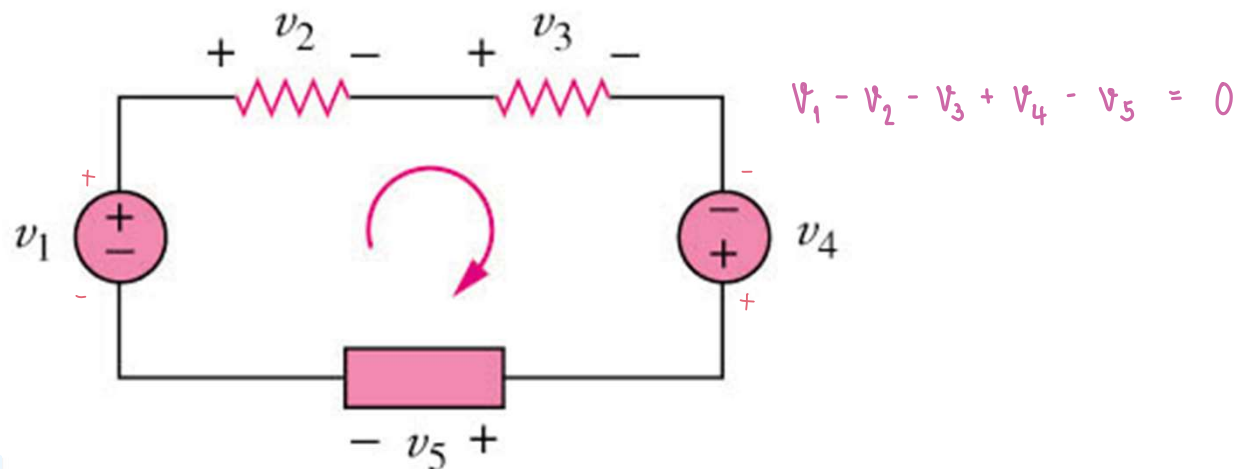2.3 Kirchhoff's Laws (3)

- Kirchhoff's voltage law (KVL) states that the algebraic sum of all voltages around a closed path (or loop) is zero.




Mathematically,

$$\sum_{m=1}^M v_n = 0$$

2.3 Kirchhoff's Laws (4)

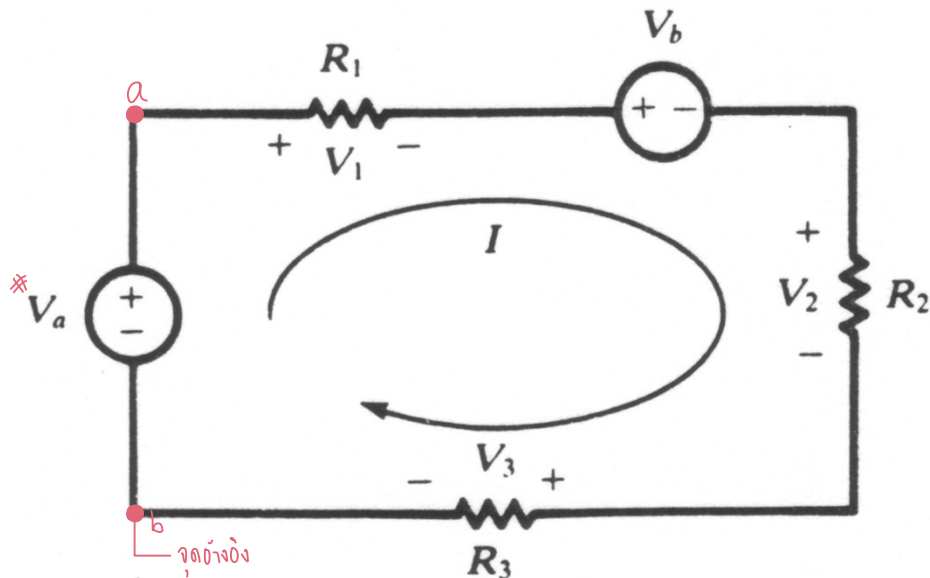
Example 5 Applying the KVL equation for the circuit of the figure below.



$$V_a - V_1 - V_b - V_2 - V_3 = 0$$

$$V_1 = IR_1 \quad V_2 = IR_2 \quad V_3 = IR_3$$
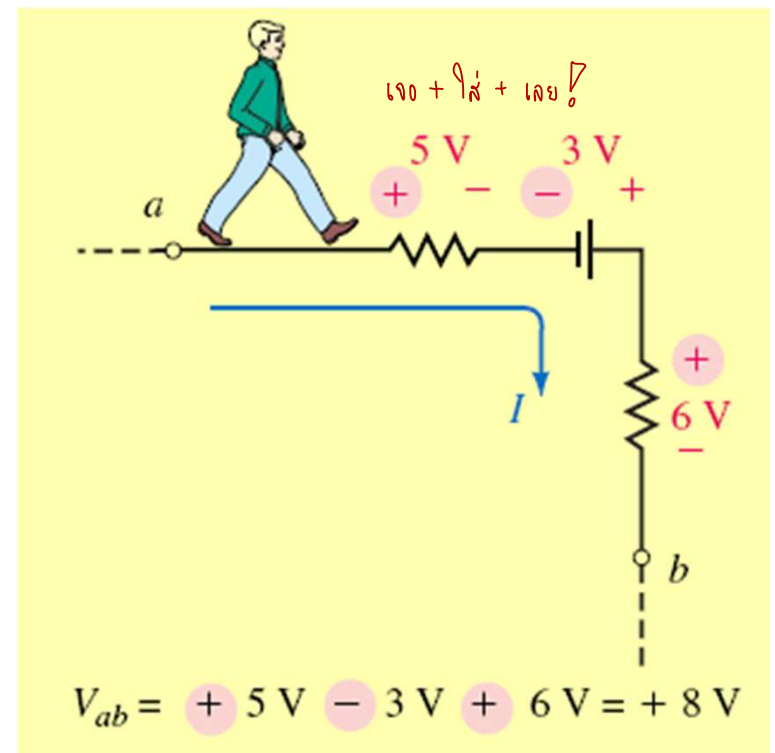
$$\Rightarrow V_a - V_b = I(R_1 + R_2 + R_3)$$



$$I = \frac{V_a - V_b}{R_1 + R_2 + R_3} \longrightarrow I = \frac{\Delta V}{\Delta R}$$

2.4 Series Resistors and Voltage Division (1)

อนุกรม


- Series: Two or more elements are in series if they are cascaded or connected sequentially and consequently carry the same current. I เท่ากัน

สมมูล

- The equivalent resistance of any number of resistors connected in a series is the sum of the individual resistances.



$$* R_{eq} = R_1 + R_2 + \cdots + R_N = \sum_{n=1}^N R_n$$

- The voltage divider can be expressed as
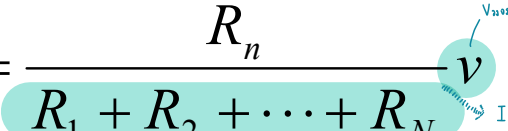
$$* v_n = \frac{R_n}{R_1 + R_2 + \cdots + R_N} V_{in}$$

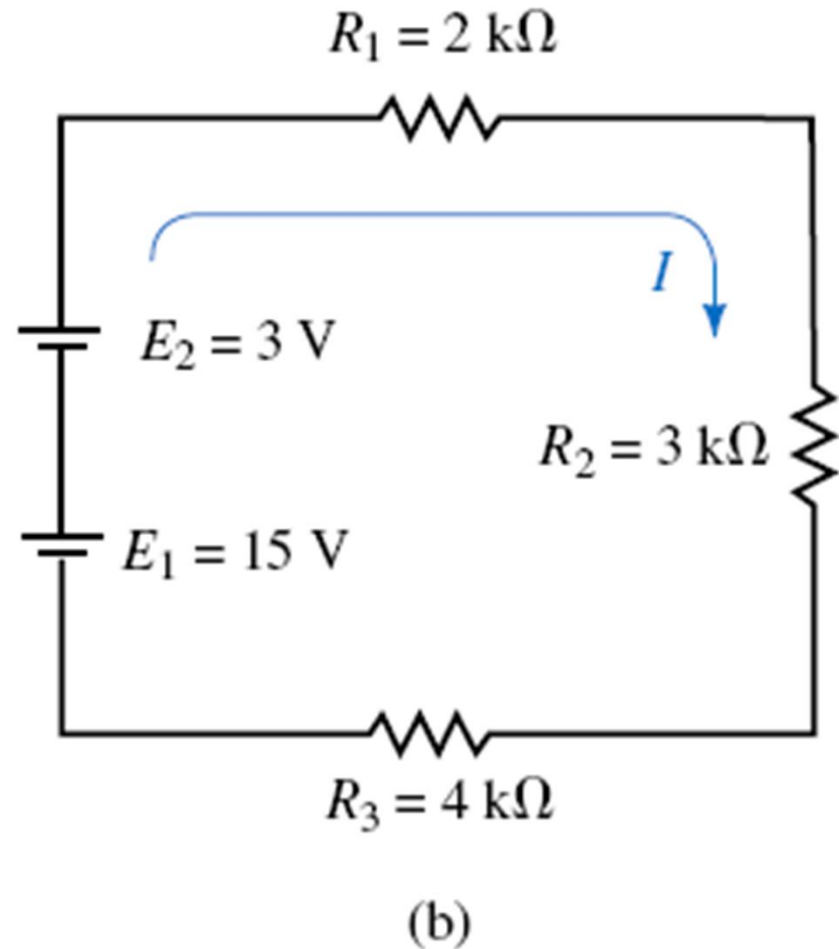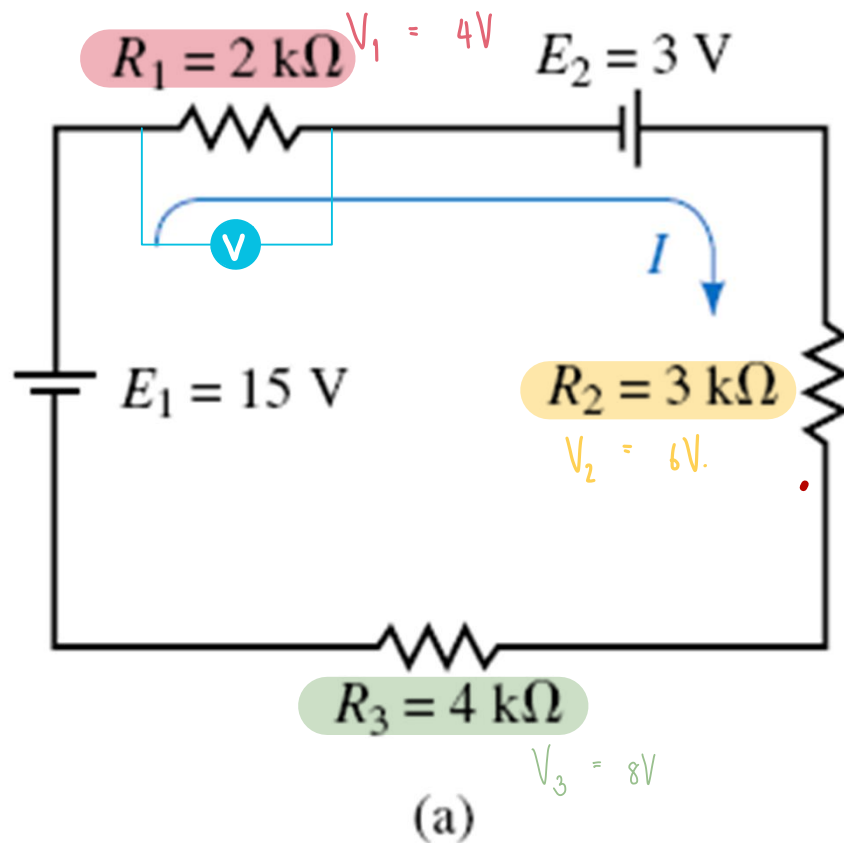
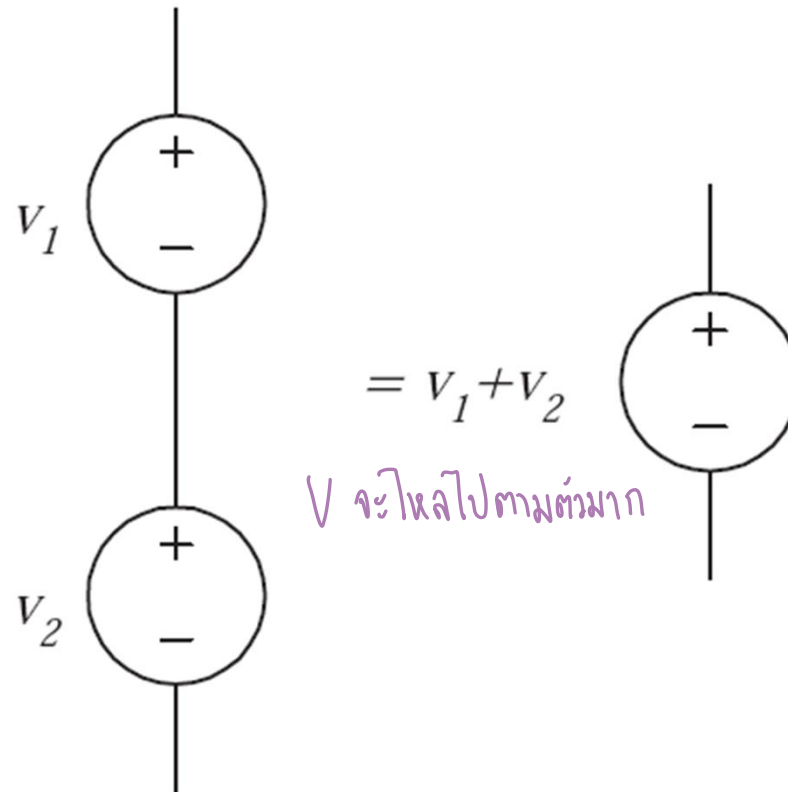
Interchanging Series Components

$$I = \frac{15 + 3 \text{ (V)}}{2\text{K} + 3\text{K} + 4\text{K}(\Omega)} = 2.0 \text{ mA}$$




* ต่ออนุกรมจะสลับที่ได้ แต่ค่า +/- เหมือนกัน

Voltage source in series



- Ideal voltage sources connected in series add


Voltage source in parallel

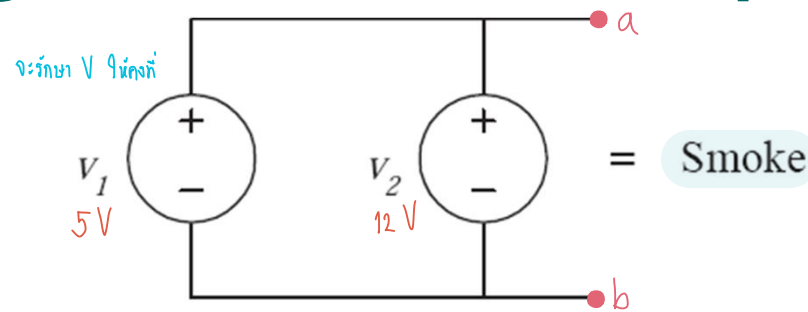

- Ideal voltage sources *cannot* be connected in parallel
- Recall: ideal voltage sources guarantee the voltage between two terminals is at the specified potential (voltage)
- Immovable object meets unstoppable force
- In practice, the stronger source would win
- Could easily cause component failure (smoke)
- Ideal sources do not exist
- Technically allowed if $V_1 = V_2$, but is a bad idea

2.4 Series Resistors and Voltage Division (1)

Example 3

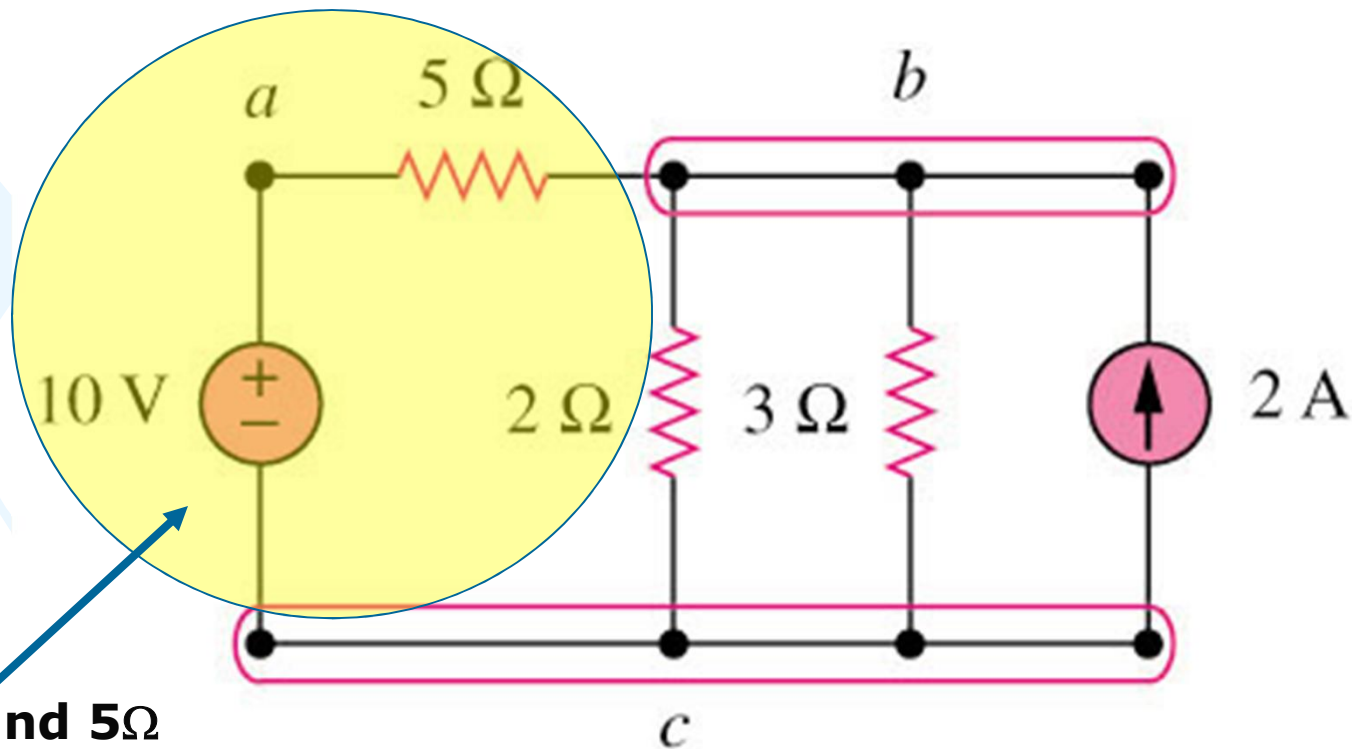

**10V and $5\ \Omega$
are in series**

2.5 Parallel Resistors and Current Division (1)


- Parallel: Two or more elements are in parallel if they are connected to the same two nodes and consequently have the same voltage across them.

- The equivalent resistance of a circuit with N resistors in parallel is:

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$


- The total current i is shared by the resistors in inverse proportion to their resistances. The current divider can be expressed as:
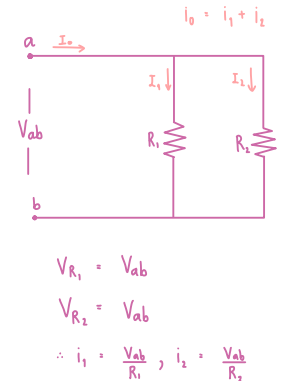
$$i_n = \frac{v}{R_n} = \frac{i R_{eq}}{R_n}$$



2.5 Parallel Resistors and Current Division (1)

Example 4

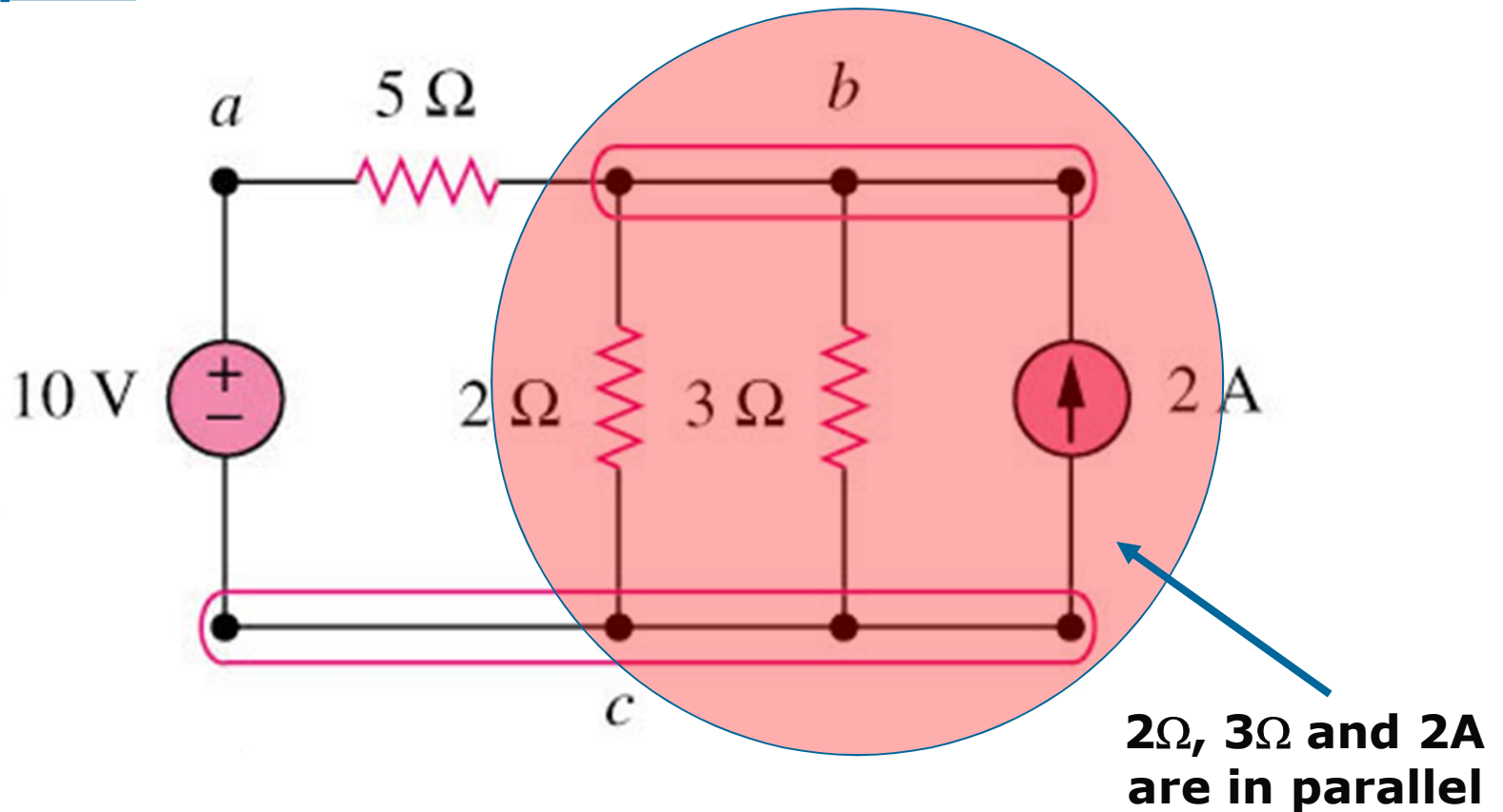


2.6 Wye-Delta Transformations

Delta -> Star

$$R_1 = \frac{R_b R_c}{(R_a + R_b + R_c)}$$

$$R_2 = \frac{R_c R_a}{(R_a + R_b + R_c)}$$
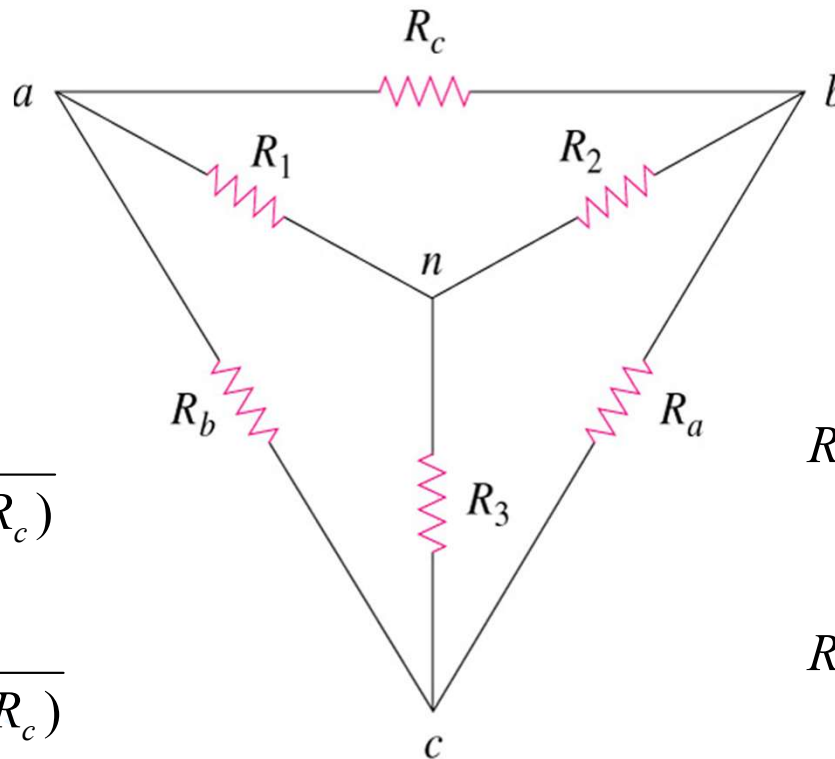
$$R_3 = \frac{R_a R_b}{(R_a + R_b + R_c)}$$




Star -> Delta

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$
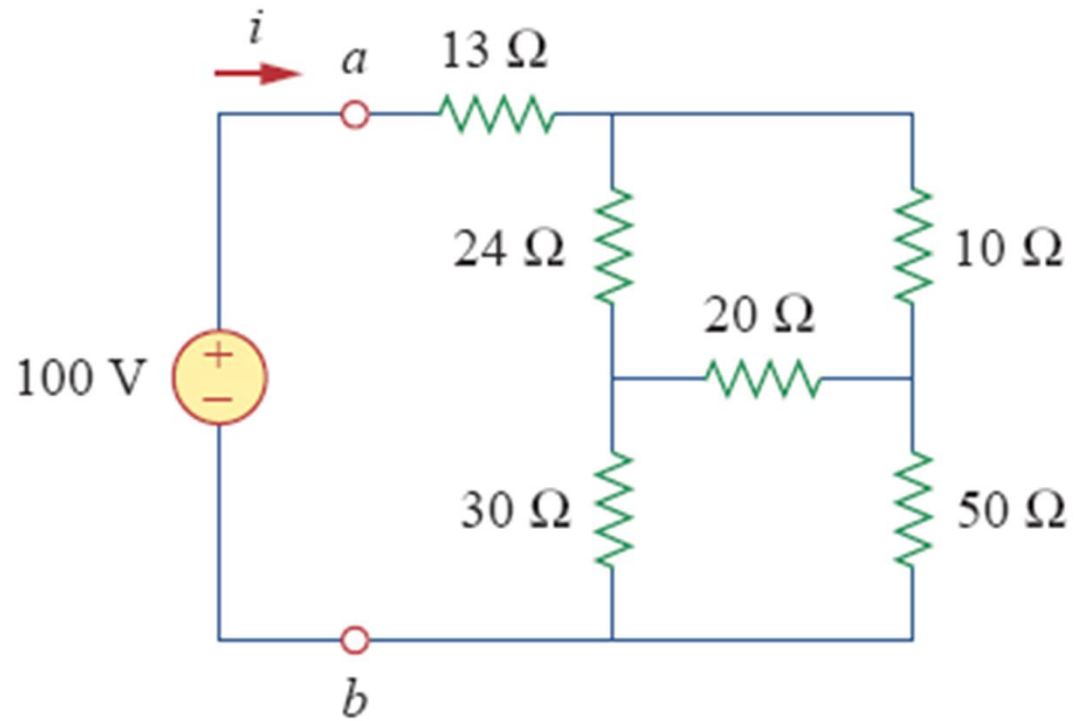
$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$



เปลี่ยนเป็น

